

ECE 545 Fall 2009

Final Exam

Introduction & tasks:

The key scheduling unit of the RC5 cipher is a circuit that takes a 128-bit key K , and converts it to $2r+2$ round keys $S[i]$, $i=0..2r+1$, stored in the internal memory $S[i]$.

This unit is specified below using its

- a. pseudocode
- b. interface
- c. table of input/output ports.

Perform the following six phases of the design process for the RC5 key scheduling unit implementation:

1. **Block diagram of the Datapath**
2. **Interface with the division into the Datapath and the Controller**
3. **ASM chart of the Controller**
4. **VHDL code of the Controller**
5. **Timing analysis**
6. **Expected-output analysis**

Pseudocode:

The RC5 key scheduling unit is defined using the given below pseudocode.

The input key K consists of four words $K[0]$, $K[1]$, $K[2]$, and $K[3]$, each of the size of 32 bits.

These words are first written to the internal memory $L[j]$, $j=0..3$, using the control signal `write_key` (active high) and the key input K_{in} . This process is described using the first `for-loop` of the pseudocode. Afterwards, the remaining part of the pseudocode is executed by the controller.

P_{32} and Q_{32} are 32-bit constants. r is a parameter of RC5, with the default value of 12.

```
for j = 0 to 3 do
    while (not write_key)
        do_nothing
    end while
    L[j] = Kin
end for
```

```
S[0] = P32
for i=1 to 2r+1 do
    S[i] = S[i-1] + Q32
end for
```

```

i = j = 0
A = B = 0
for k=1 to 3 · (2r+2) do
    A' = S[i] = (S[i] + A + B) <<< 3
    B' = L[j] = (L[j] + A' + B) <<< (A'+B)
    A = A'
    B = B'
    i = (i+1) mod (2r+2)
    j = (j+1) mod 4
end for

```

Notation:

A, B, A', B' = 32-bit variables

+ = unsigned addition mod 2^{32}


$X \ll Y$ = rotation of the variable X by a number of positions given by the current value of the variable Y

Assume that you can use memories with the following inputs:
 ADDR, DIN, CLK, WE, and the output DOUT,
 which output data in the same clock cycle in which a new address is applied.

Writing to memory takes effect at the rising edge of the clock when WE = 1.

Interface:

 Assume the following interface to your circuit:



Port	Width	Meaning
clk	1	System clock.
reset	1	System reset - clears internal registers.
write_key	1	Synchronous write control signal for the key input, Kin. Active high.
Kin	32	The key input, through which subsequent words of the key K[0]..K[3] are loaded to the circuit.

n	m	Index n of the round key S[n].
Sn	w	Value of the round key S[n] corresponding to the index provided through the input n.
Done	1	Asserted when the computations are completed.

m is a size of index n. It is a minimum integer, such that $2^m \geq 2r+2$.

Tasks & Assumptions:

Task 1: Draw a block diagram of the Datapath

Assume that

- one round of the main for loop of the pseudocode executes in one clock cycle
- you can access only one position of each internal memory per clock cycle
- after the circuit is done with computations, applying input n should generate value of S[n] at the output Sn in the same clock cycle.

Task 2: Draw an Interface of the circuit with the division into the Datapath and the Controller

Task 3: Draw an ASM chart of a controller capable of performing computations described in the pseudocode.

Task 4: Write synthesizable VHDL code of the controller defined in Task 3.

Assume that:

- values of the parameters r and m are specified as constants or generics.

Task 5: Write formulas for the

- latency of your circuit as a function of the minimum clock period, and
- minimum clock period in terms of delays of basic logic components shown in your block diagram

Mark the critical path of your circuit on its block diagram.

Task 6:

Draw timing waveforms showing all inputs and outputs from the controller, as well as its internal state during

- first 6 clock cycles after reset becomes inactive (assume that the write_key signal becomes active immediately after reset goes low)
- first 6 clock cycles of the main (third) for-loop of the pseudocode.