

**ECE 545**



**Midterm Exam**

**Fall 2013**







**Solutions**

# Problem 1


	15	12	11	8	7	4	3	0
Range 0:	0000	0	0	XXX	XXXX	XXXX		
Range 1:	0000	1	XXX	XXXX	XXXX			
Range 2:	0001	0	XXX	XXXX	XXXX			
Range 3:	0001	1	XXX	XXXX	XXXX			
Range 4:	0010	0	XXX	XXXX	XXXX			

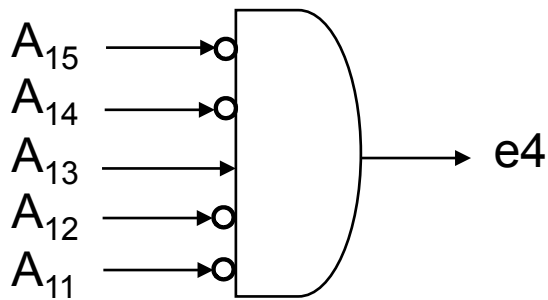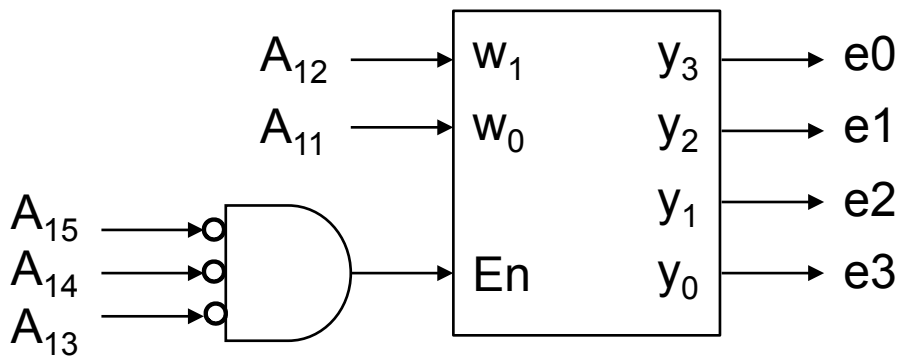


# Problem 2

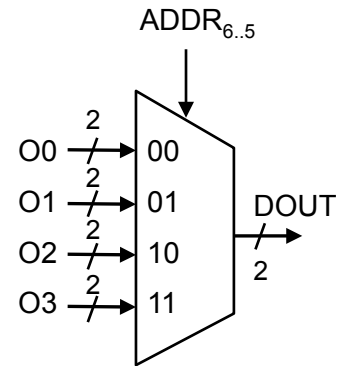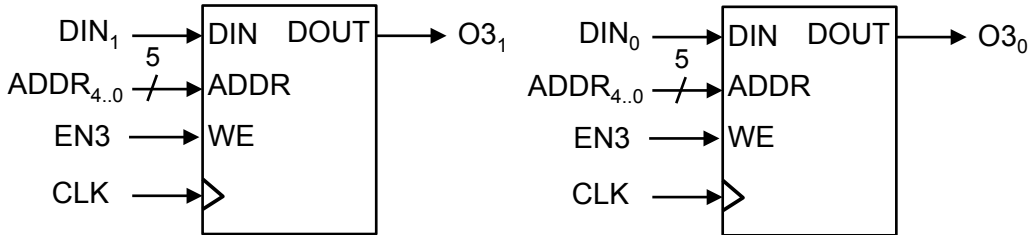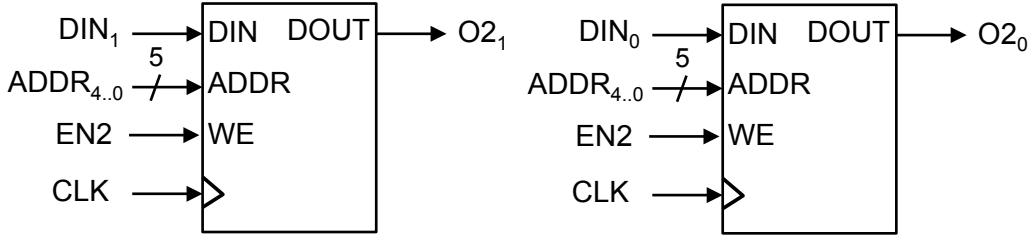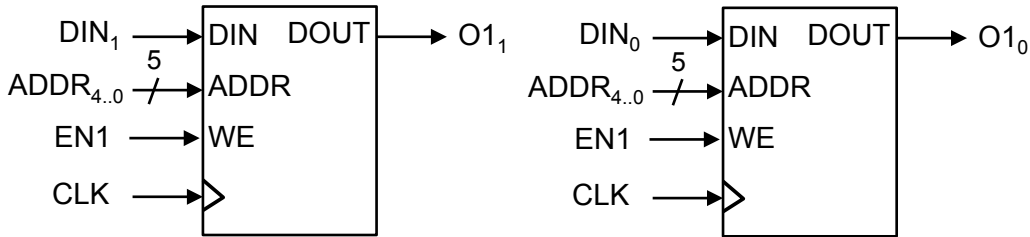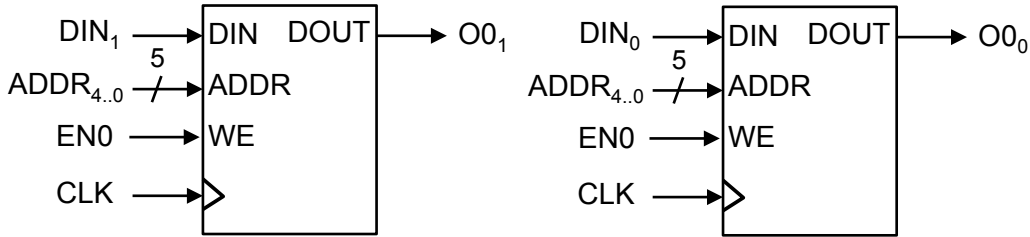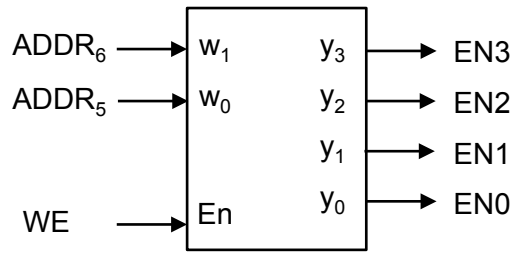

# Problem 3 – Task 1

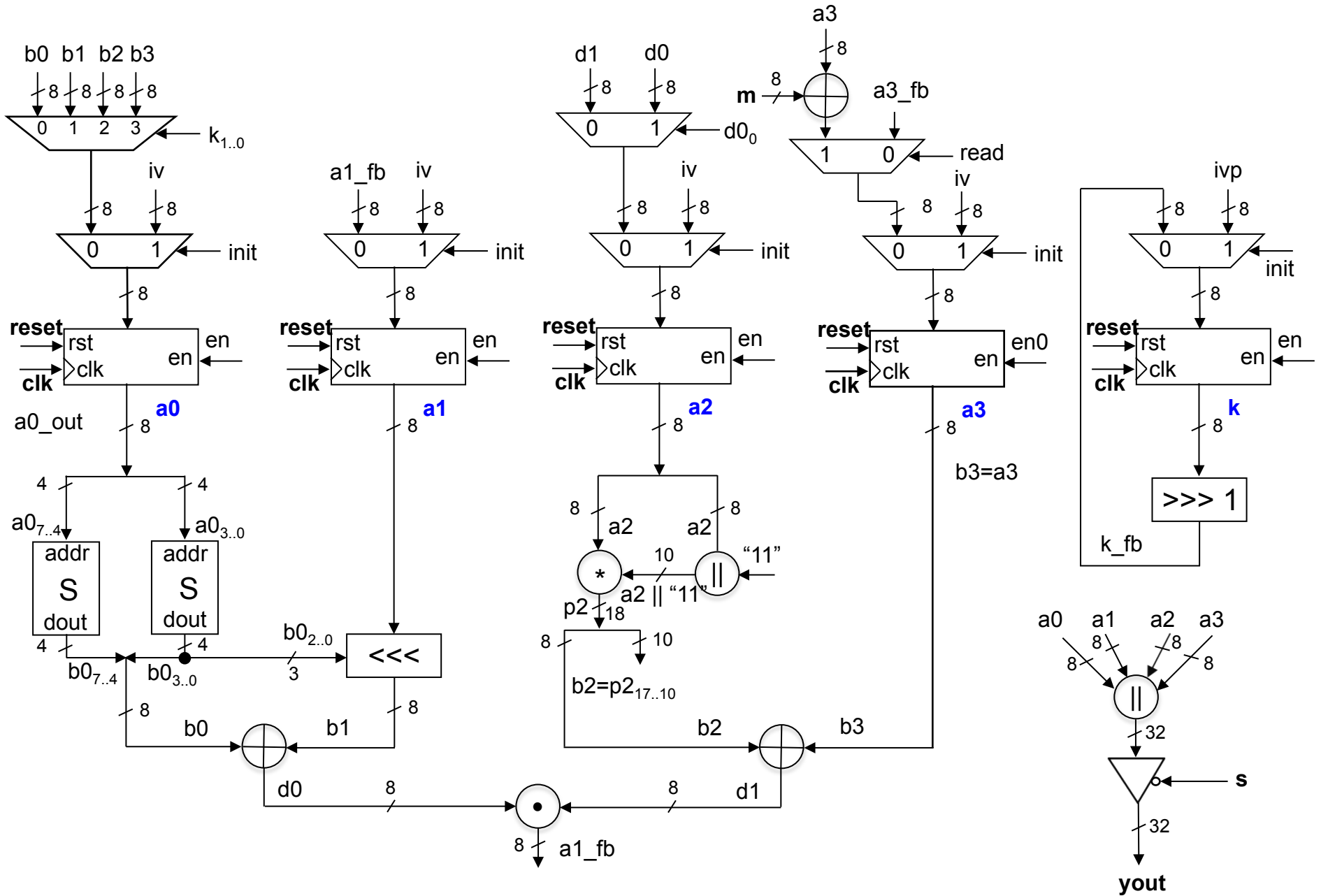

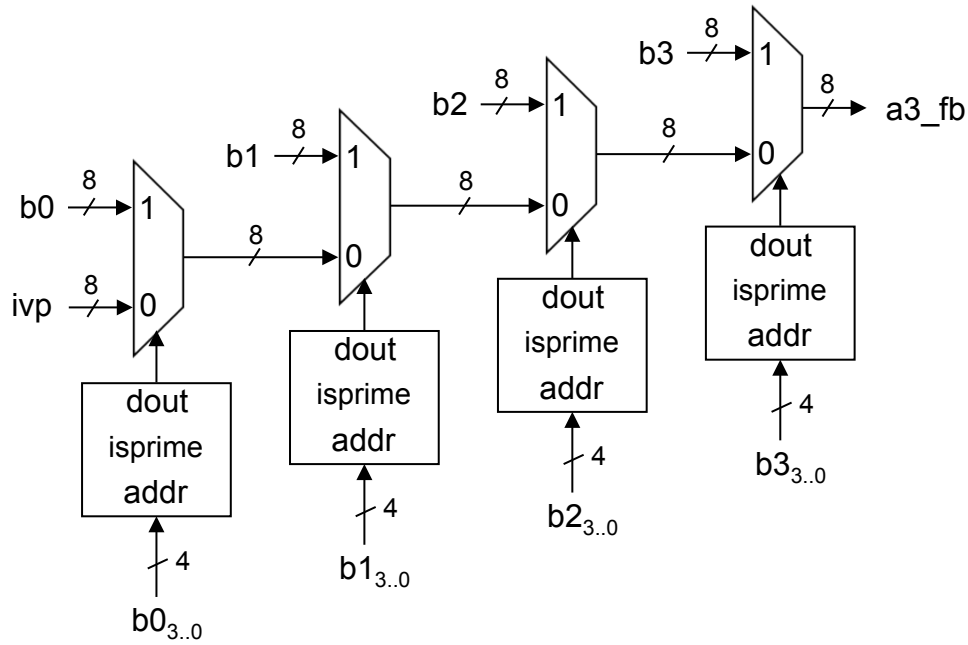

## Optimizations:

$$b3 = (8 * a3 \oplus 6) \gg 3 =$$




$$= (a3 \parallel \text{"110"}) \gg 3 = a3$$

$$k = 0 \parallel k_{7..1} \text{ if } k_0 = 0$$

$$k = 1 \parallel k_{7..1} \text{ if } k_0 = 1$$


thus,
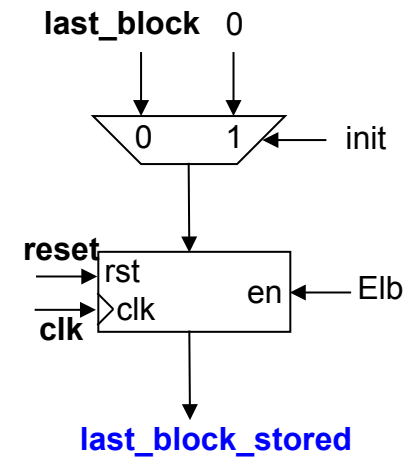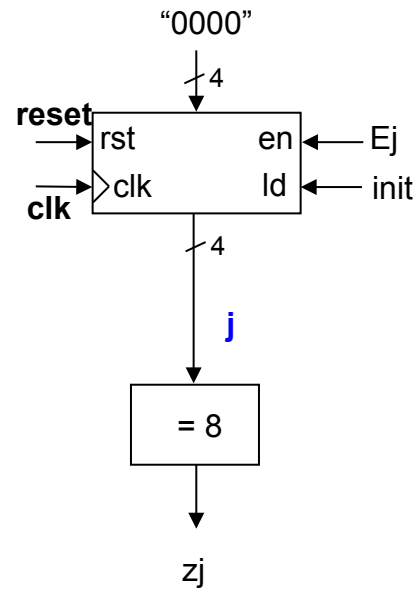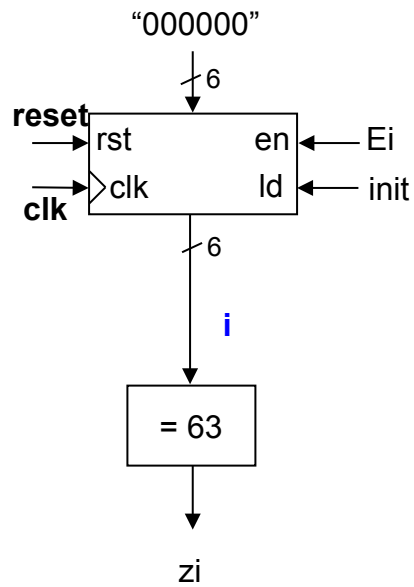
$$k = k_0 \parallel k_{7..1} = k \gg \gg 1$$




### Problem 3 – Task 2

a) Substitution  $Y=S[X]$

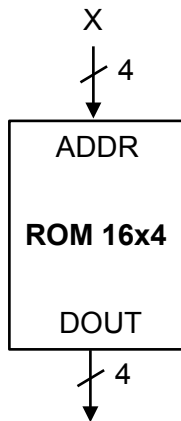


0	E
1	D
2	B
3	0
4	2
5	1
6	4
7	F
8	7
9	A
10	8
11	5
12	9
13	C
14	3
15	6

b) Function  $Y=isprime[X]$

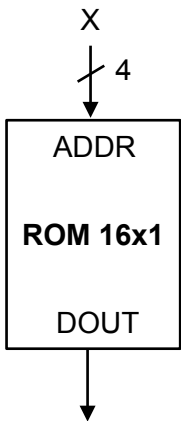

0	0
1	0
2	1
3	1
4	0
5	1
6	0
7	1
8	0
9	0
10	0
11	1
12	0
13	1
14	0
15	0

### Problem 3 – Task 3

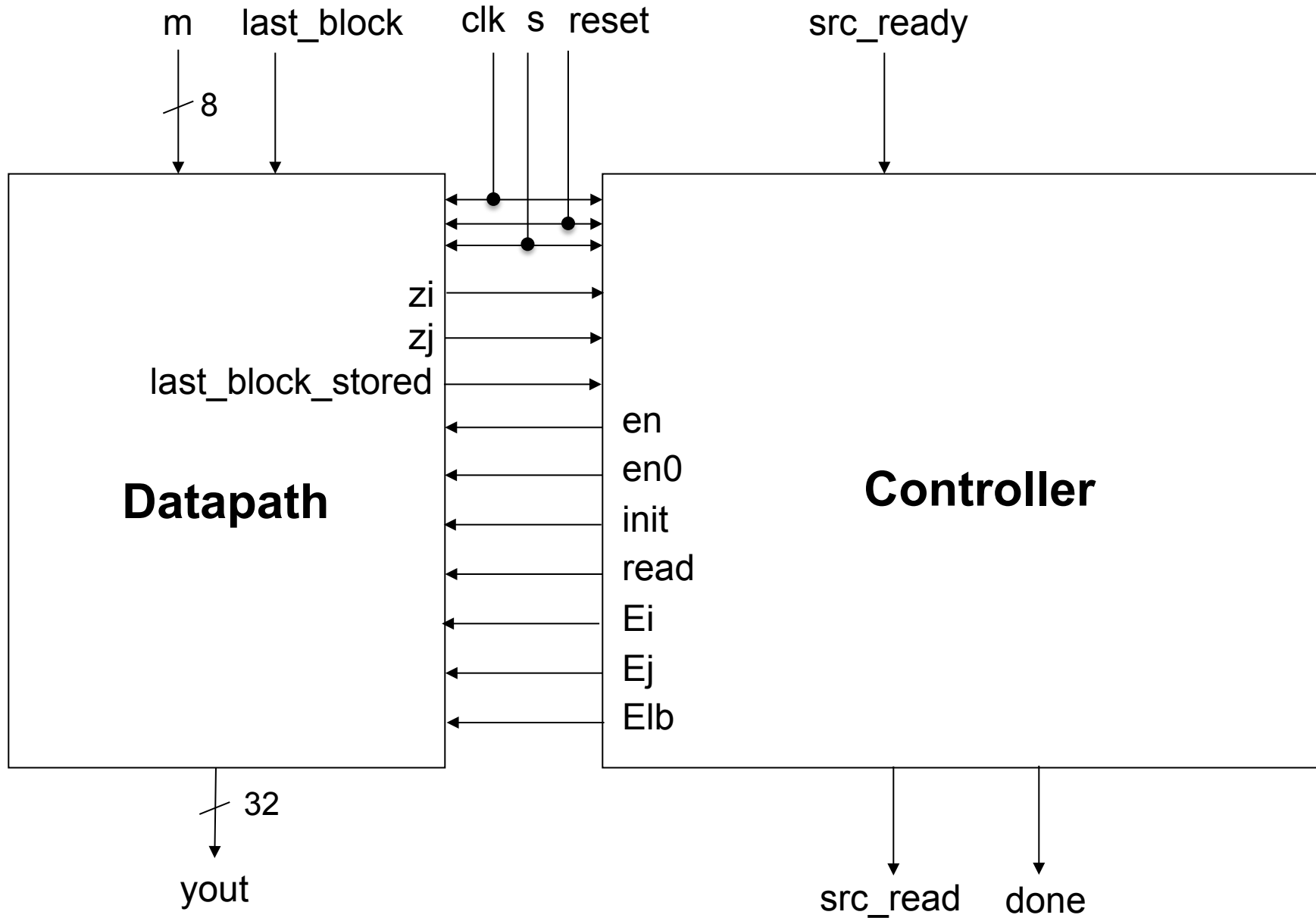

## Problem 4

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity misr is  
  generic (C : std_logic_vector(7 downto 0) );  
  port (  
    -- inputs  
    clk   : in   std_logic;  
    rst   : in   std_logic;  
    en    : in   std_logic;  
    D     : in   std_logic_vector (7 downto 0);  
  
    -- outputs  
    Q_out: out  std_logic_vector (7 downto 0)  
  );  
end misr;
```

```
architecture mixed of misr is
```

```
-- intermediate signals  
signal Q : std_logic_vector (7 downto 0);  
signal Q0_replicated : std_logic_vector (7 downto 0);  
signal d_ff_in : std_logic_vector (7 downto 0);
```

```
begin
```

```
  Q0_replicated <= (others => Q(0));  
  d_ff_in <= D xor ('0' & Q(7 downto 1)) xor (C and Q0_replicated);
```

```
-- D flip flop operation  
  D_FF: process (rst, clk)  
  begin  
    if (rst = '1') then  
      Q <= (others => '0');  
    elsif rising_edge(clk) then  
      if(en = '1') then  
        Q <= d_ff_in;  
      end if;  
    end if;  
  end process;
```

```
  Q_out <= Q;  
end mixed;
```