

Lecture 8

FPGA Multipliers

Radix 2 Sequential Multipliers

Required Reading

Behrooz Parhami,

Computer Arithmetic: Algorithms and Hardware Design

Chapter 9, Basic Multiplication Scheme

Chapter 10, High-Radix Multipliers

Chapter 12.3, Bit-Serial Multipliers

Chapter 12.4, Modular Multipliers

FPGA Multipliers

Notation

Y	Multiplicand	$Y_{k-1} Y_{k-2} \dots Y_1 Y_0$
X	Multiplier	$X_{m-1} X_{m-2} \dots X_1 X_0$
P	Product (Y · X)	$p_{m+k-1} p_{m+k-2} \dots p_2 p_1 p_0$

If multiplicand and multiplier are of different sizes,
usually multiplier has the smaller size

Xilinx FPGA Implementation Equations

$$Z = (2x_{m-1} + x_{m-2}) \cdot Y \cdot 2^{m-2} + \dots + (2x_{i+1} + x_i) \cdot Y \cdot 2^i + \dots + \\ +(2x_3 + x_2) \cdot Y \cdot 2^2 + (2x_1 + x_0) \cdot Y \cdot 2^0$$

$$(2x_{i+1} + x_i) \cdot Y = p_{i(k+1)} p_{ik} p_{i(k-1)} \dots p_{i2} p_{i1} p_{i0}$$


$$p_{ij} = x_i \cdot y_j \text{ xor } x_{i+1} \cdot y_{j-1} \text{ xor } c_j$$

$$c_{j+1} = (x_i \cdot y_j)(x_{i+1} \cdot y_{j-1}) + (x_i \cdot y_j) \cdot c_j + (x_{i+1} \cdot y_{j-1}) \cdot c_j$$

$$c_0 = c_1 = 0$$

Modified Basic Cell


Xilinx FPGA Implementation

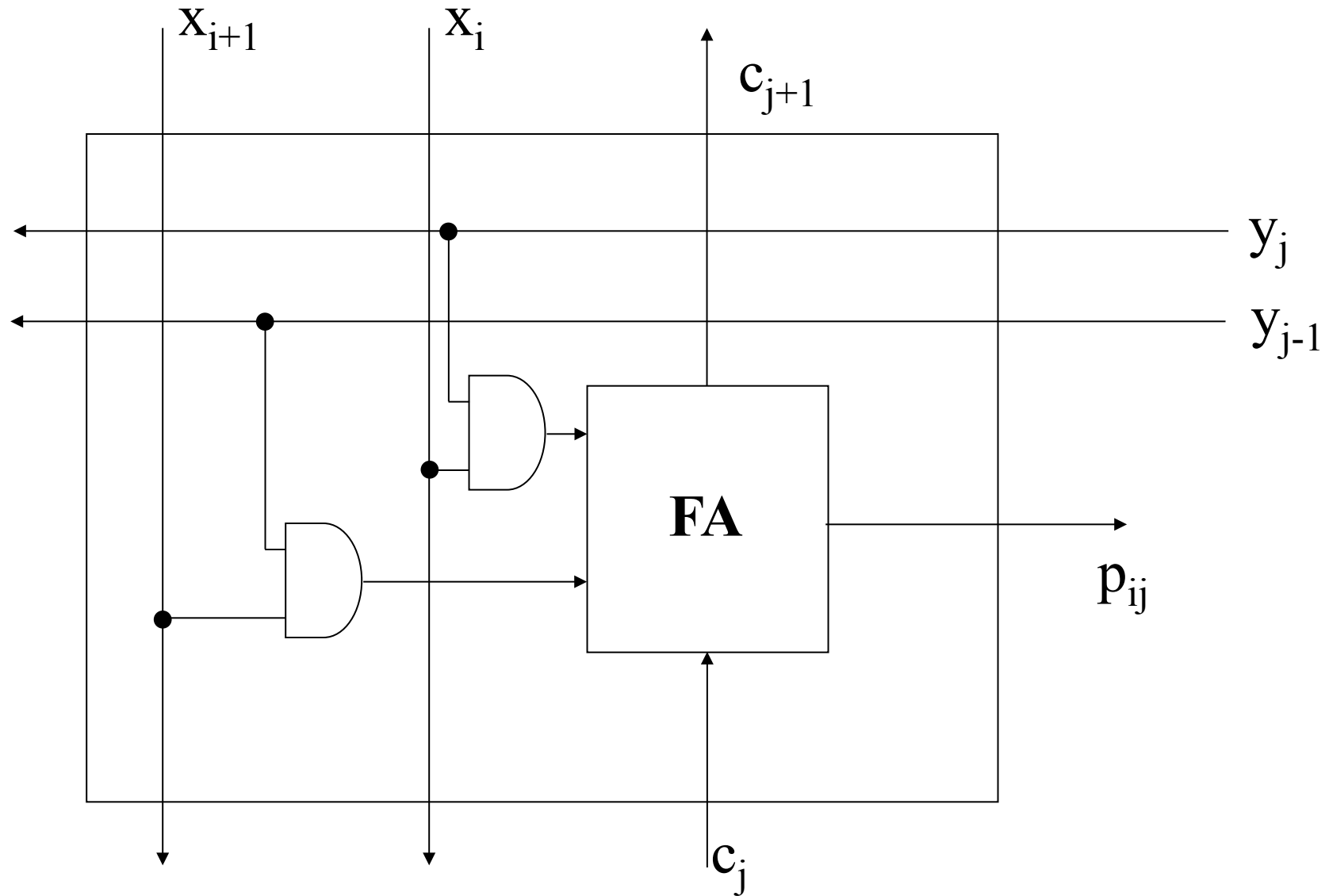

Modified Basic Cell

Xilinx FPGA Implementation

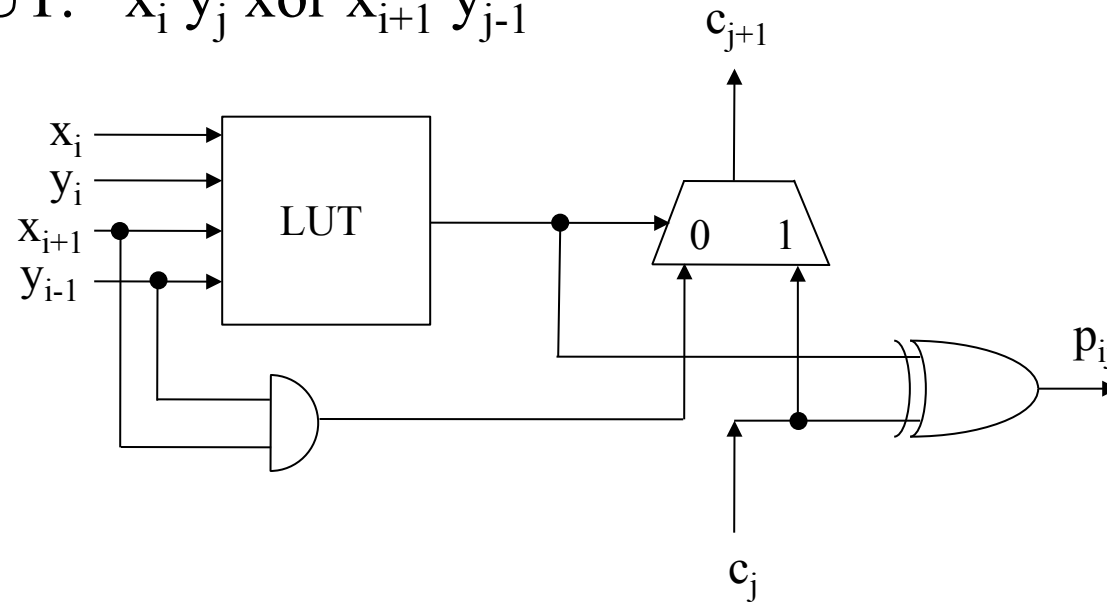
LUT: $x_i \cdot y_j \text{ xor } x_{i+1} \cdot y_{j-1}$



$$p_{ij} = x_i \cdot y_j \text{ xor } x_{i+1} \cdot y_{j-1} \text{ xor } c_j$$

$$c_{j+1} = (x_i \cdot y_j)(x_{i+1} \cdot y_{j-1}) + (x_i \cdot y_j) \cdot c_j + (x_{i+1} \cdot y_{j-1}) \cdot c_j$$

Xilinx FPGA Multiplier

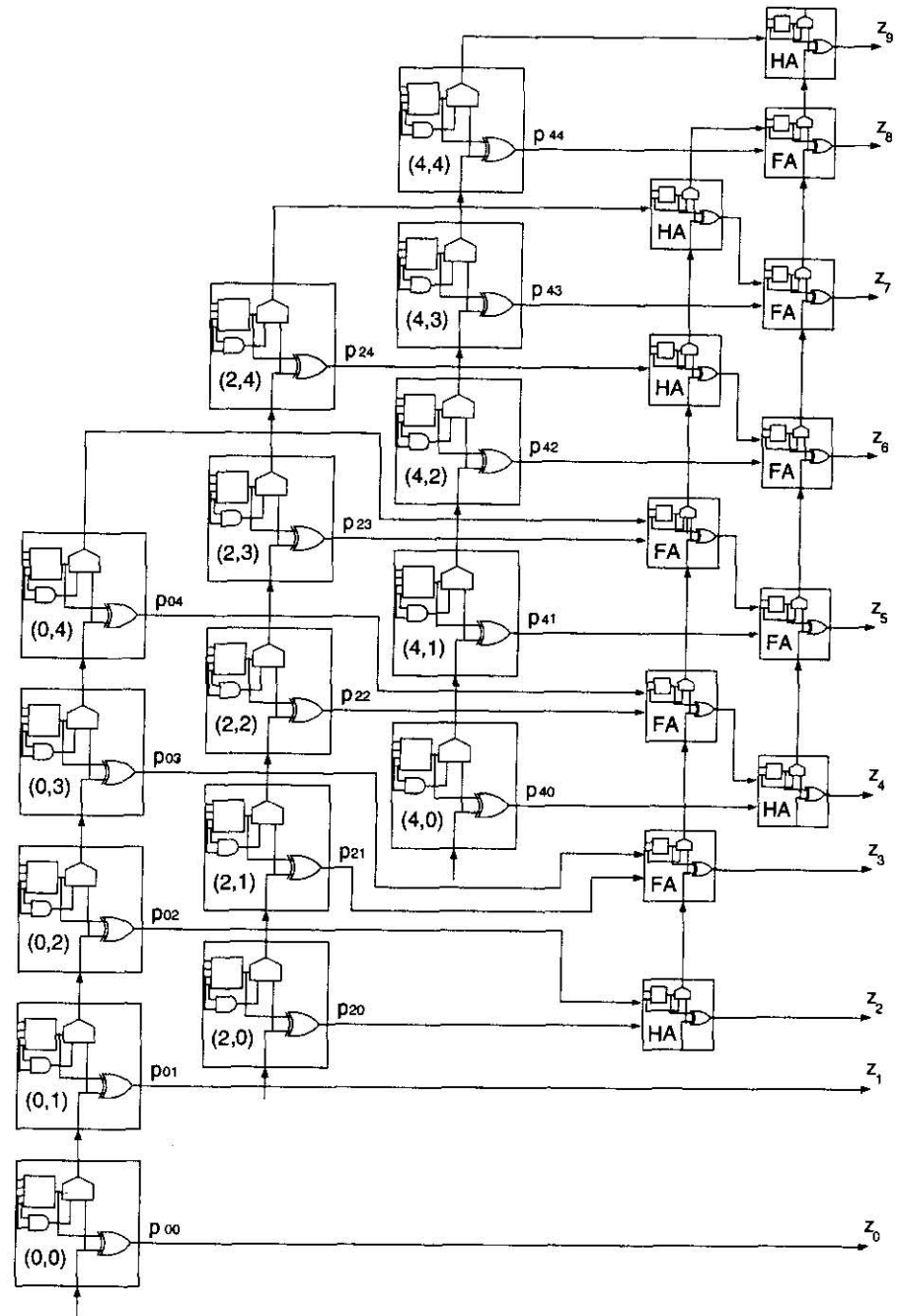


Radix 2 Sequential Multipliers

Notation

a	Multiplicand	$a_{k-1} a_{k-2} \dots a_1 a_0$
x	Multiplier	$x_{k-1} x_{k-2} \dots x_1 x_0$
p	Product (a · x)	$p_{2k-1} p_{2k-2} \dots p_2 p_1 p_0$

If multiplicand and multiplier are of different sizes,
usually multiplier has the smaller size

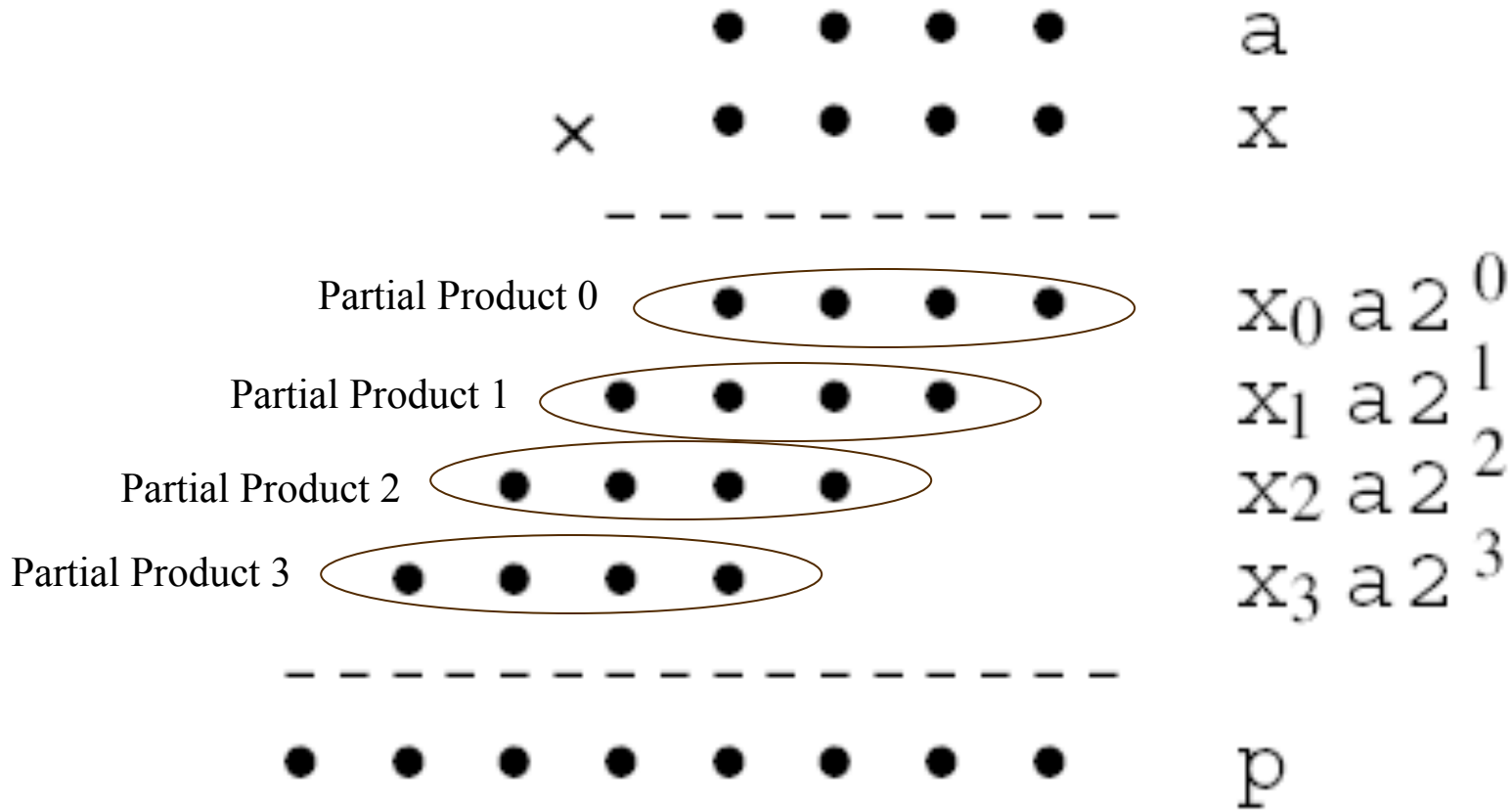Multiplication of two 4-bit unsigned binary numbers in dot notation



Number of partial products = number of bits in multiplier x
Bit-width of each partial product = bit-width of multiplicand a

Basic Multiplication Equations

$$p = a \cdot x \qquad x = \sum_{i=0}^{k-1} x_i \cdot 2^i$$

$$\begin{aligned} p = a \cdot x &= \sum_{i=0}^{k-1} a \cdot x_i \cdot 2^i = \\ &= x_0 a 2^0 + x_1 a 2^1 + x_2 a 2^2 + \dots + x_{k-1} a 2^{k-1} \end{aligned}$$

Shift/Add Algorithm

Right-shift version

Shift/Add Algorithms

Right-shift algorithm

$$p = a \cdot x = x_0 a 2^0 + x_1 a 2^1 + x_2 a 2^2 + \dots + x_{k-1} a 2^{k-1} =$$

$$= \underbrace{(\dots((0 + x_0 a 2^k)/2 + x_1 a 2^k)/2 + \dots + x_{k-1} a 2^k)/2}_{k \text{ times}} =$$


k times

$$p^{(0)} = 0$$

$$p^{(j+1)} = (p^{(j)} + x_j a 2^k) / 2 \quad j=0..k-1$$

$$p = p^{(k)}$$

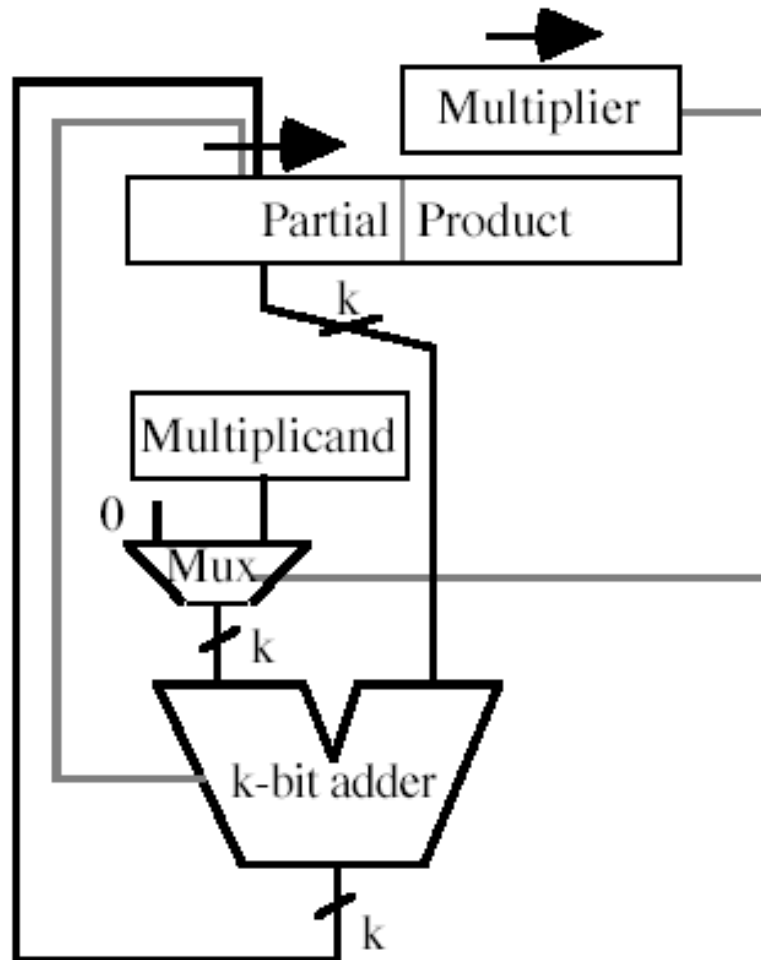Sequential shift-and-add multiplier for right-shift algorithm



Right-shift multiplication algorithm: Example

Right-shift algorithm

=====	
a	1 0 1 0
x	1 0 1 1
=====	
$p^{(0)}$	0 0 0 0
$+x_0a$	1 0 1 0


$2p^{(1)}$	0 1 0 1 0
$p^{(1)}$	0 1 0 1 0
$+x_1a$	1 0 1 0

$2p^{(2)}$	0 1 1 1 1 0
$p^{(2)}$	0 1 1 1 1 0
$+x_2a$	0 0 0 0

$2p^{(3)}$	0 0 1 1 1 1 0
$p^{(3)}$	0 0 1 1 1 1 0
$+x_3a$	1 0 1 0

$2p^{(4)}$	0 1 1 0 1 1 1 0
$p^{(4)}$	0 1 1 0 1 1 1 0
=====	

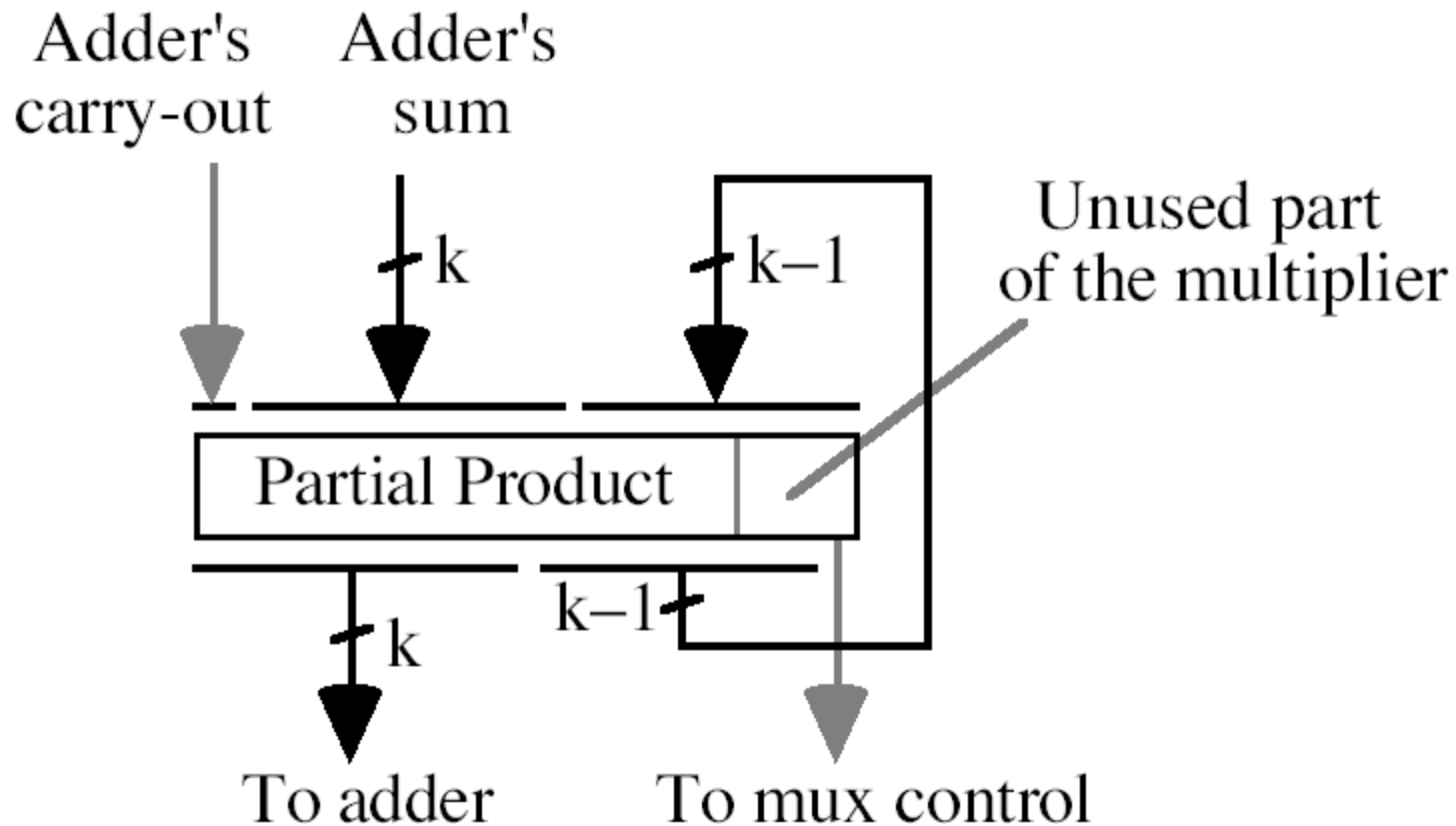Area optimization for the sequential shift-and-add multiplier with the right-shift algorithm



Shift/Add Algorithms

Right-shift algorithm: multiply-add

$$p^{(0)} = y2^k$$

$$p^{(j+1)} = (p^{(j)} + x_j a 2^k) / 2 \quad j=0..k-1$$

$$p = p^{(k)}$$

$$= \underbrace{(\dots((y2^k + x_0 a 2^k) / 2 + x_1 a 2^k) / 2 + \dots + x_{k-1} a 2^k) / 2}_{k \text{ times}} =$$

k times

$$= y + x_0 a 2^0 + x_1 a 2^1 + x_2 a 2^2 + \dots + x_{k-1} a 2^{k-1} = y + a \cdot x$$

Signed Multiplication

- Previous sequential multipliers are for unsigned multiplication
- For signed multiplication:
 - assume sign-extended operation for $p^{(j)} + x_j a$
 - if 2's complement multiplier is POSITIVE
right-shift sequential algorithms (shift-add) will work directly
 - if 2's complement multiplier is NEGATIVE than we must use "negative weight" for x_{k-1} and subtract $x_{k-1} a$ in the last cycle
- Slight increase in area due to control and one-bit sign extension on inputs of adder
 - Unsigned: k bit number + k bit number \rightarrow k+1 bit number
 - Signed: k+1 bit sign extended number + k+1 bit sign extended number \rightarrow k+1 bit number

**Sequential
multiplication
of 2' s-complement
numbers
with right shifts
(positive multiplier)**

=====							
a		1	0	1	1	0	
x		0	1	0	1	1	
=====							
$p^{(0)}$		0	0	0	0	0	
$+x_0a$		1	0	1	1	0	

$2p^{(1)}$	1	1	0	1	1	0	
$p^{(1)}$		1	1	0	1	1	0
$+x_1a$		1	0	1	1	0	

$2p^{(2)}$	1	1	0	0	0	1	0
$p^{(2)}$		1	1	0	0	0	1
$+x_2a$		0	0	0	0	0	

$2p^{(3)}$	1	1	1	0	0	0	1
$p^{(3)}$		1	1	1	0	0	0
$+x_3a$		1	0	1	1	0	

$2p^{(4)}$	1	1	0	0	1	0	0
$p^{(4)}$		1	1	0	0	1	0
$+x_4a$		0	0	0	0	0	

$2p^{(5)}$	1	1	1	0	0	1	0
$p^{(5)}$		1	1	1	0	0	1
=====							

**Sequential
multiplication
of 2's-complement
numbers
with right shifts
(negative multiplier)**

a	1 0 1 1 0
x	1 0 1 0 1
=====	
$p^{(0)}$	0 0 0 0 0
$+x_0a$	1 0 1 1 0

$2p^{(1)}$	1 1 0 1 1 0
$p^{(1)}$	1 1 0 1 1 0
$+x_1a$	0 0 0 0 0

$2p^{(2)}$	1 1 1 0 1 1 0
$p^{(2)}$	1 1 1 0 1 1 0
$+x_2a$	1 0 1 1 0

$2p^{(3)}$	1 1 0 0 1 1 1 0
$p^{(3)}$	1 1 0 0 1 1 1 0
$+x_3a$	0 0 0 0 0

$2p^{(4)}$	1 1 1 0 0 1 1 1 0
$p^{(4)}$	1 1 1 0 0 1 1 1 0
$+(-x_4a)$	0 1 0 1 0

$2p^{(5)}$	0 0 0 1 1 0 1 1 1 0
$p^{(5)}$	0 0 0 1 1 0 1 1 1 0
=====	

Shift/Add Algorithm

Left-shift version

Shift/Add Algorithms

Left-shift algorithm

$$p = a \cdot x = x_0 a 2^0 + x_1 a 2^1 + x_2 a 2^2 + \dots + x_{k-1} a 2^{k-1} =$$

$$= \underbrace{(\dots((0 \cdot 2 + x_{k-1} a) \cdot 2 + x_{k-2} a) \cdot 2 + \dots + x_1 a) \cdot 2 + x_0 a}_{k \text{ times}}$$


k times

$$p^{(0)} = 0$$

$$p^{(j+1)} = (p^{(j)} \cdot 2 + x_{k-1-j} a) \quad j=0..k-1$$

$$p = p^{(k)}$$

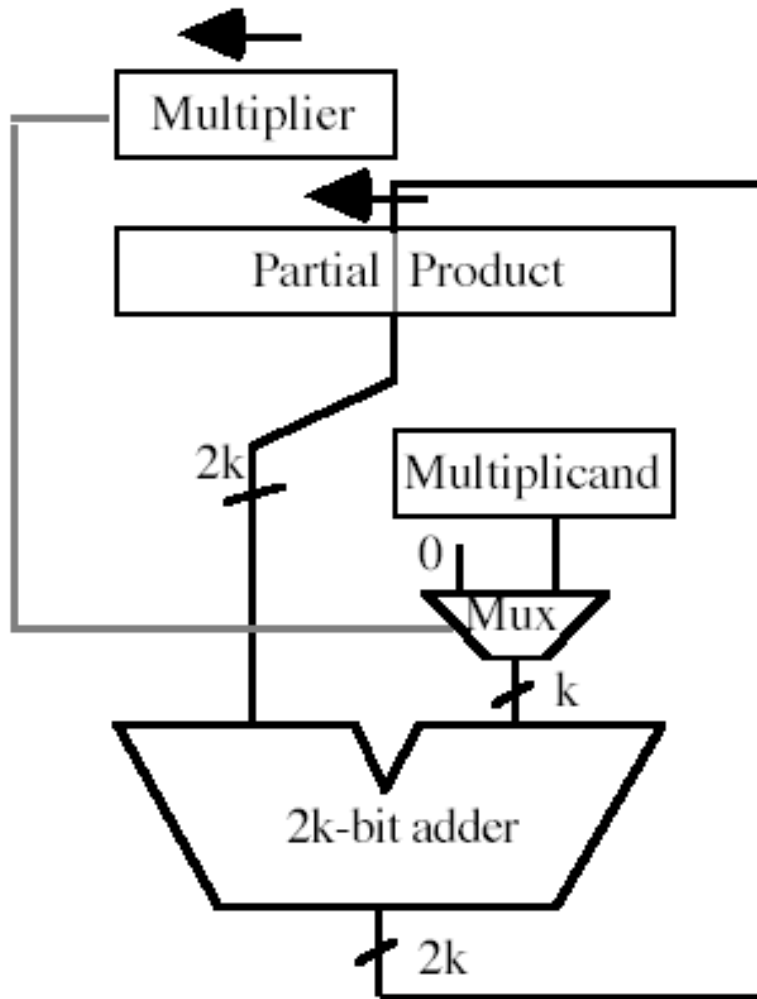Sequential shift-and-add multiplier for left-shift algorithm



Left shifts are not as efficient for two's complement because must sign extend multiplicand by k bits

Left-shift multiplication algorithm: Example

Left-shift algorithm

=====				
a				1 0 1 0
x				1 0 1 1
=====				
$p^{(0)}$				0 0 0 0
$2p^{(0)}$	0			0 0 0 0
$+x_3a$				1 0 1 0

$p^{(1)}$	0			1 0 1 0
$2p^{(1)}$	0 1			0 1 0 0
$+x_2a$				0 0 0 0

$p^{(2)}$	0 1			0 1 0 0
$2p^{(2)}$	0 1 0			1 0 0 0
$+x_1a$				1 0 1 0

$p^{(3)}$	0 1 1			0 0 1 0
$2p^{(3)}$	0 1 1 0			0 1 0 0
$+x_0a$				1 0 1 0

$p^{(4)}$	0 1 1 0			1 1 1 0
=====				

Shift/Add Algorithms

Left-shift algorithm: multiply-add

$$p^{(0)} = y2^{-k}$$

$$p^{(j+1)} = (p^{(j)} \cdot 2 + x_{k-(j+1)}a) \quad j=0..k-1$$

$$p = p^{(k)}$$

$$= \underbrace{(\dots((y2^{-k} \cdot 2 + x_{k-1}a) \cdot 2 + x_{k-2}a) \cdot 2 + \dots + x_1a) \cdot 2 + x_0a}_{k \text{ times}} =$$

$$= y + x_{k-1}a2^{k-1} + x_{k-2}a2^{k-2} + \dots + x_1a2^1 + x_0a = y + a \cdot x$$

Shift/Add Algorithm
Right-shift version
with Carry-Save Adder

Sequential shift-and-add multiplier with a carry save adder

