

# Homework 9: Due Tuesday April 10<sup>th</sup> (10:30 am, beginning of class)

---

Write your name at the top of each page.

- Start a **new page for each problem**.
  - **Order** and **staple** your pages.
  - Always complete the reading assignments *before* attempting the homework problems.
  - Show all of your work. Use written English, where applicable, to provide a log of your steps in solving a problem. (For numerical homework problems, the writing can be brief.)
  - A solution which requires physical units is *incorrect* unless the units are listed in the result.
  - Underline, circle or box your result.
  - Always write neatly. Communication skills are essential in engineering and science. If neither the TA nor the instructor can read it, you will receive zero points.
- 

## 1) Terminal Characteristics and Interfacing

- a) Determine the fanout limit when a Texas Instruments SN7400 (Quad 2-Input NAND) drives an ON Semiconductor SN74LS00 (Quad 2-Input NAND). For the SN74LS00, assume  $V_{IN}=2.7$  V when determining  $I_{IH}$ , if needed. The data sheet for the Texas Instruments part can be found on the class website.
- b) Determine the fanout limit when an ON Semiconductor SN74LS00 (Quad 2-Input NAND) drives a Texas Instruments SN7400 (Quad 2-Input NAND). For the SN74LS00, assume  $V_{IN}=2.7$  V when determining  $I_{IH}$ , if needed.

## 2) Power Dissipation

For each IC listed below, determine the quiescent power dissipation, dynamic power dissipation and total power dissipation when one gate from each IC drives a capacitive load of  $CL = 15$  pF at switching frequencies of 100 kHz, 1 MHz and 10 MHz at  $V_{CC} = 5$  V. Assume the gate output is HIGH 3/4 of the time and LOW 1/4 of the time. All the necessary data sheets can be found on the class website.

- a) ON Semiconductor 74LS283
- b) Philips 74F283
- c) Philips 74HC283