

# ECE 545 Midterm Exam Fall 2004

November 11, 2004

## Problem

### Function


Design and describe using RTL VHDL a circuit capable of calculating the minimum, maximum, and average of  $k$   $n$ -bit numbers, for any values of  $k$  and  $n$  which are the powers of 2, e.g.  $k=8$  and  $n=32$ .

### Optimization

Optimize your circuit for the minimum total execution time. When choosing between two circuits with the same or very similar execution time, give preference to the circuit with the smaller area.
 
### Interface

Assume the following interface to your circuit:



Port	Width	Meaning
clk	1	System clock
reset	1	System reset – clears internal registers
in_data	$n$	Input data bus
in_addr	$m=\log_2 k$	Address of the internal memory where input data is stored
write	1	Synchronous write control signal
START	1	Starts the computations
DONE	1	Asserted when all results are ready
out_data	$n$	Output data bus used to read results
out_addr	2	01 – reading minimum 10 – reading maximum 11 – reading average 00 – high impedance at the output data bus
read	1	Synchronous read control signal

### *Verification*

Verify your circuit using functional simulation for the case of  $k=8$  and  $n=32$  using a testbench capable of reading input data from a text file in the hexadecimal notation, and writing output data to a text file in the hexadecimal notation.

### *Synthesis & implementation*

Synthesize and implement your circuit for the two cases:  $\{k=8, n=32\}$  and  $\{k=16, n=64\}$ , targeting the smallest device of the Spartan 2 family capable of holding both circuits.

Based on the implementation reports, determine for each case:

- a. circuit area in the number of CLB slices
- b. minimum clock period
- c. worst case execution time (from START to DONE), assuming the use of the minimum clock period.

### *Timing simulation*

Verify the operation of your circuit for the case of  $k=8$  and  $n=32$  using timing simulation at the minimum clock period.

### **Suggested design steps**

1. Draw a block diagram of the execution unit of your circuit
2. Draw a block diagram of a part of the control unit of your circuit
3. Describe the remaining portion of the control unit using ASM chart
4. Translate ASM chart from actions to values of specific control signals
5. Describe an interface to your circuit in VHDL
6. Translate block diagrams designed in steps 1 and 2 to VHDL
7. Translate the final ASM chart obtained in step 4 to VHDL
8. Write a testbench capable of simulating your circuit
9. Verify the operation of your circuit using functional simulation, introduce corrections in your code if necessary
10. Synthesize and implement your circuit.
11. Determine circuit area, minimum clock period, and worst case execution time based on the implementation reports.
12. Verify the operation of your circuit using timing simulation at the minimum clock period.

### **Deliverables**

#### *Handwritten on paper:*

1. All block diagrams you have developed
2. All ASM charts you have developed

#### *Electronic version (TO BE SUBMITTED BY WEBCT):*

1. All source codes describing your circuit
2. All testbench files, including input and corresponding output files
3. A short text or MS Word file describing circuit area, minimum clock period, and worst case execution time.
4. Waveforms from the functional and timing simulations.