

ECE 545 Fall 2010
Final Exam

Introduction & tasks:

The MD-5 hash function circuit is specified below using its:

- a. pseudocode
- b. interface
- c. table of input/output ports
- d. timing requirements (in the description of Task 1).

Perform the following 5 phases of the design process for the MD-5 implementation:

- 1. Block diagram of the Datapath**
- 2. Interface with the division into the Datapath and the Controller**
- 3. ASM chart of the Controller**
- 4. VHDL code of the Controller**
- 5. Analysis of the possible use of embedded resources**

Pseudocode:

```
//Initialize hash result:
var int h0 := iv0
var int h1 := iv1
var int h2 := iv2
var int h3 := iv3

//Process the message in successive 512-bit blocks:
for each 512-bit block of the message
    break the block into sixteen 32-bit words w[j], 0 ≤ j ≤ 15

    //Initialize the state for the block:
    var int a := h0
    var int b := h1
    var int c := h2
    var int d := h3

    //Main loop:
    for i from 0 to 63
        if 0 ≤ i ≤ 15 then
            f := (b and c) or ((not b) and d)
            g := i
        else if 16 ≤ i ≤ 31
            f := (d and b) or ((not d) and c)
            g := (5*i + 1) mod 16
        else if 32 ≤ i ≤ 47
            f := b xor c xor d
            g := (3*i + 5) mod 16
        else if 48 ≤ i ≤ 63
            f := c xor (b or (not d))
            g := (7*i) mod 16
        end if

        temp := d
        d := c
        c := b
        b := b + leftrotate((a + f + k[i] + w[g]), r[i])
        a := temp
    end for
```

```

//Add the state to the hash result so far:
h0 := h0 + a
h1 := h1 + b
h2 := h2 + c
h3 := h3 + d
end for

digest := h0 || h1 || h2 || h3

```

Notation:

All variables, except *i*, *g*, *r[i]*, and *digest*, represent 32-bit words.

iv0..iv3 : initialization vector

h0..h3 : intermediate hash result

digest: hash value

k[i] : round constant, specific to each round. All round constants are precomputed and stored in a Block RAM operating in a single-port ROM mode.

w[j]: message block words

not : one's complement of a 32-bit word.

xor, and, or : Boolean operations on 32-bit words.

leftrotate(a, r) : rotation of the variable **a** by **r** positions to the left

r[i]: rotation amount specific to a given round. Rotation amounts are specified below, and are assumed to be stored in a distributed ROM.

r[0..15]:={7, 12, 17, 22, 7, 12, 17, 22, 7, 12, 17, 22, 7, 12, 17, 22}

r[16..31]:={5, 9, 14, 20, 5, 9, 14, 20, 5, 9, 14, 20, 5, 9, 14, 20}

r[32..47]:={4, 11, 16, 23, 4, 11, 16, 23, 4, 11, 16, 23, 4, 11, 16, 23}

r[48..63]:={6, 10, 15, 21, 6, 10, 15, 21, 6, 10, 15, 21, 6, 10, 15, 21}

a || b: a concatenated with b

Interface:

Assume the following interface to your circuit:

 


Table of input/output ports:

Port	Width	Meaning
clk	1	System clock.
reset	1	System reset – clears all internal register in the datapath and resets control unit.
mi	32	Message input. Message blocks are read from the source one word at a time.
hn	32	Hash value output. The hash value is written to the destination one word at a time.
src_ready	1	Input control signal indicating that the source of data is ready with the next message word.
src_read	1	Output control signal indicating reading the next message word from the source of data.
dst_ready	1	Input control signal indicating that the destination of data is ready to receive the next output word.
dst_write	1	Output control signal indicating writing the next output word to the destination of data.
last_block	1	Input control signal indicating that the last word of the message is being read.
done	1	Set to '1' when the entire hash value was written to the destination.

Tasks & Assumptions:

Task 1 [30 points]: Draw block diagram of the Datapath of the circuit

Assume that

- the target FPGA device is Spartan 3
- round constants are kept in a single-port embedded ROM
- rotation constants are kept in a distributed ROM
- one clock cycle is used for the once-per-message initialization:
 $h_0 = iv_0; h_1 = iv_1; h_2 = iv_2; h_3 = iv_3;$
- one clock cycle is used for the once-per-block initialization:
 $a = h_0; b = h_1; c = h_2; d = h_3;$
- one round of the main for loop of the pseudocode executes in one clock cycle;
there are a total of 64 rounds.
- one clock cycle is used for the once-per-block finalization:
 $h_0 = h_0 + a; h_1 = h_1 + b; h_2 = h_2 + c; h_3 = h_3 + d;$

As a result, hashing of the message M, consisting of N 512-bit blocks (each block=16 32-bit words) should last $1+(1+64+1)*N$ clock cycles. The hash value is then written to the destination circuit in 4 additional clock cycles.

Please clearly mark the widths and directions of all buses in your block diagram.

Task 2 [10 points]: Draw an interface between the Control Unit and the Datapath

Show the names and widths of all signals forming this interface.

Task 3 [30 points]: Draw an ASM chart of a controller capable of performing computations described in the pseudocode. Translate each action and condition in your ASM chart to the values of the corresponding control and status signals.

Task 4 [20 points]: Write synthesizable VHDL code of the controller defined in Task 3. You can write architecture only, no need for entity declaration.

Task 5 [10 points]:

Assuming the maximum use of embedded resources available in Spartan 3 FPGAs, how many embedded resources of each type can be used to implement MD 5 in Spartan 3? In case of block memories, please specify the configuration (address size and output size of a Block RAM) and the actual size of the memory portion used to store data).

How would you go about specifying the use of these resources in your VHDL code?

- Please choose and shortly describe one method.
- Please provide a short justification (a list of advantages) of the selected method.