

**ECE 545 Fall 2013
Midterm Exam**

Problem 1 [10 points]

Show how to implement an address decoder that recognizes the following five ranges of the 16-bit address A, and generates the corresponding enable signals e0-e4, indicating that the address is in the given range:

Range 0: 0000-07FF
Range 1: 0800-0FFF
Range 2: 1000-17FF
Range 3: 1800-1FFF
Range 4: 2000-27FF

Problem 2 [15 points]

Given eight 32x1 RAMs and basic combinational logic components, show (using a block diagram) how to build a single 128x2 RAM.

Assume that all RAMs have only the following ports: ADDR (address), DIN (data in), WE (write enable), CLK (clock), and DOUT (data out).

In your block diagram, clearly specify

- names, widths and directions of all buses
- names, widths and directions of all inputs and outputs of logic components.

Problem 3 [60 points]

The **EXAM** function is specified below using its:

- a. Pseudocode
- b. Table of input/output ports
- c. Timing requirements.

1. Pseudocode:

```
begin:
wait for s=1

a0 := iv
a1 := iv
a2 := iv
a3 := iv
k := ivp
j := 0
last_block_stored :=0

do
  if (last_block_stored /= 1) then
    wait until src_ready
    last_block_stored := last_block
    a3 := a3 ⊕ m
  end if
```

```

for i from 0 to 63 do
  b(0) := S[a0/16] || S[a0 mod 16]
  b(1) := a1 <<< S[a0 mod 16]
  b(2) := a2 * (4*a2+3) / 210
  b(3) := (8*a3 ⊕ 6) >> 3
  a0 := b(k mod 4)
  d0 := b(0) ⊕ b(1)
  d1 := b(2) ⊕ b(3)
  a1 := d0 · d1
  if (d0 is odd)
    a2 := d0
  else
    a2 := d1
  if ((b(3) mod 16) is prime)
    a3 := b(3)
  elsif ((b(2) mod 16) is prime)
    a3 := b(2)
  elsif ((b(1) mod 16) is prime)
    a3 := b(1)
  elsif ((b(0) mod 16) is prime)
    a3 := b(0)
  else
    a3 := ivp;
  if (k0=0)
    k := k>>1
  else
    k :=(k>>1) ⊕ (k0 << 7)
  end if
end for

if (last_block_stored = 1) then
  j++
end if;

until ((last_block_stored = 1) and (j=8))

wait for s=0
y := a0 || a1 || a2 || a3
go to begin

```

Notation:

m: 8-bit message block (input)

y: 32-bit circuit output (output)

iv, ivp : 8-bit initialization vectors (constants), iv='76', ivp='0B' (in hexadecimal notation)

a0..a3, b(0)..b(3), k, d0, d1 : 8-bit intermediate values, treated as 8-bit unsigned integers

k₀: bit 0 of k

Operations:

X ⊕ Y : bitwise XOR

X · Y : bitwise AND

X + Y : addition

X * Y : multiplication

X || Y : X concatenated with Y

X/16: integer part of the result of division of X by 16

X <<< Y : rotation of X to the left by the number of positions given in Y
X >>> Y : rotation of X to the right by the number of positions given in Y
X << Y : logical shift of X to the left by the number of positions given in Y
X >> Y : logical shift of X to the right by the number of positions given in Y

Y = S[X] : substitution defined using the following table (all values in the hexadecimal notation):

X	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
Y	E	D	B	0	2	1	4	F	7	A	8	5	9	C	3	6

2. Table of input/output ports:

Port	Mode	Width	Function
clk	Input	1	System clock.
reset	Input	1	Asynchronous system reset.
s		1	Operating mode: 0 = waiting for data / reading results, 1 = processing.
m	Input	8	8-bit message block.
src_ready	Input	1	Control signal indicating that the source is ready. Must remain active until source is read.
src_read	Output	1	Control signal confirming that the source was read. Active for one clock cycle.
last_block	Input	1	Control signal indicating the last block of the message.
done	Output	1	Control signal indicating that the output is ready.
yout	Output	32	32-bit output block y when s=0, high impedance otherwise.

3. Timing Requirements:

Assume that

- **one clock cycle is used for the once-per-message initialization:**
a0 := iv; a1 := iv; a2 := iv; a3 := iv; k := ivp
- **one round of the main for-loop of the pseudocode executes in one clock cycle;**
there are a total of 64 rounds.

Tasks:

Task 1: Block Diagram [45 points]

Draw a block diagram of the datapath of the EXAM circuit using medium complexity components corresponding to the operations used in the pseudocode.

Your Datapath should

- be capable of executing the entire pseudocode given in point 1,**
- match interface given in point 2, and**
- meet all timing requirements specified in point 3.**

Clearly specify

- **names, widths and directions of all buses**
- **names, widths and directions of all inputs and outputs of the logic components.**

Assume that one round of the main for-loop of the pseudocode executes in one clock cycle. Minimize the number of control signals to be generated by the Control Unit.

Task 2: Substitution S and the function “Is prime” [5 points]

Explain in detail your implementation of the substitution function $Y=S[X]$. Which logic component do you use to implement this function? How is this component initialized?

Show in detail your implementation of the function “Is prime”, which checks whether a given number between 0 and 15 is prime.

Assume that this function returns

1 if the input is a prime number, and returns

0 for the inputs 0 and 1, and for all composite numbers greater or equal to 2.

Task 3: Interface [10 points]

Draw an interface of the EXAM circuit, with the division into the Datapath and Controller. Show the names, widths, and directions of all signals forming this interface.

Problem 4 [15 points]

Fill in the blanks in the code of MISR (Multiple Input Signature Register), **provided in the answer sheet**. Do not write this code from scratch! The block diagram of MISR is shown in figure below. Assume that the circuit has an asynchronous reset.

