

**ECE 545
Fall 2014
Midterm Exam**

Problem 1 [10 points]

Draw a block diagram of a simple microprocessor system, composed of

- A. Microprocessor, with the bidirectional input/output DATA (8-bits), and outputs ADDR (16 bits), WR (1 bit), RD (1 bit)
- B. 16k x 8 RAM0 visible by the microprocessor in the address range 0000-3FFF
- C. 16k x 8 RAM1 visible by the microprocessor in the address range 4000-7FFF
- D. 16k x 8 RAM2 visible by the microprocessor in the address range 8000-BFFF
- E. 16k x 8 RAM3 visible by the microprocessor in the address range C000-FFFF.

Assume that a memory write cycle is indicated by the microprocessor with an active value of the output WR, and a memory read cycle with an active value of the output RD.

Problem 2 [15 points]

Fill in the blanks in the code of the Debouncer circuit, **provided in the answer sheet**. **Do not write this code from scratch!** The block diagram of the Debouncer is shown in Fig. 1.

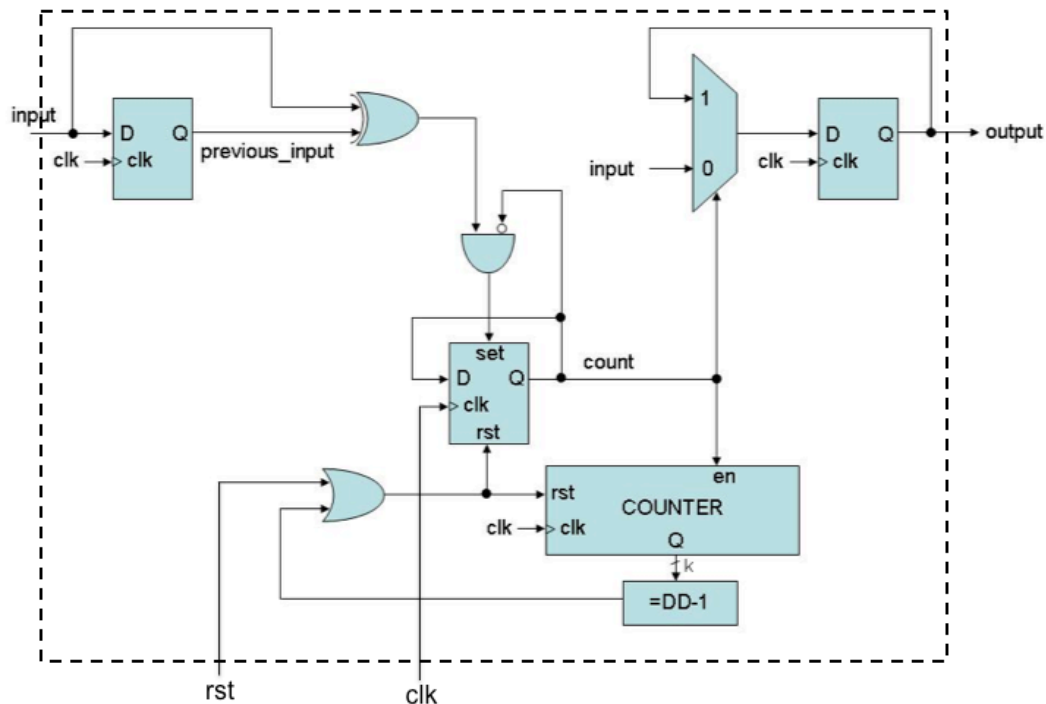


Fig. 1: Block diagram of the Debouncer circuit.

Problem 3 [15 points]

Write a complete simple testbench capable of testing the debouncer shown in Fig. 1, by applying

- A. clk, B. rst, C. input shown in Fig. 2.
- The clock signal, clk, should be a periodical signal, with the period of 10 ns.
 - The reset signal, rst, should be a non-periodical signal, active high for the first 50 ns of the simulation period.
 - The input signal should look as shown in Fig. 2, and should have all changes happening on the falling edges of the clock.
 - The Debouncer, shown in Fig. 1, should be instantiated with the following values of the generics k and DD: k = 4, DD = 15.

 


Fig. 2: Timing waveform of the input signal.

Problem 4 [60 points]

The **EXAM** function is specified below using its:

- a. Pseudocode
- b. Table of input/output ports
- c. Functional and timing requirements.

1. Pseudocode:

DES Encryption, $C = E_K(M)$:

```
X = IP(M)
L(0) = X1..32
R(0) = X33..64
for i = 0 to 15 do
    L(i+1) = R(i)
    R(i+1) = L(i) ⊕ f(R(i), K(i))
end for
Y = R(16) || L(16)
C = IP-1(Y)
```

DES Decryption, $M = D_K(C)$:

```
X = IP(C)
R(16) = X1..32
L(16) = X33..64
```

```

for i = 15 downto 0 do
    R(i) = L(i+1)
    L(i) = R(i+1) ⊕ f(L(i+1), K(i))
end for
Y = L(0) || R(0)
M = IP-1(Y)

```

Function f, Z = f(R, K):


```

U = E(R) ⊕ K
for i = 0 to 7 do
    V(i) = Ui+6+1..i+6+6
    W(i) = Sbox(V(i))
end for
Z = W(0) || W(1) || W(2) || W(3) || W(4) || W(5) || W(6) || W(7)

```


Both encryption and decryption should be able to operate in the CBC mode, shown conceptually in the diagrams below:

 **Cipher Block Chaining Mode - CBC
Encryption**



$$c_i = E_K(m_i \oplus c_{i-1}) \quad \text{for } i=1..N \quad c_0=IV$$

 **Cipher Block Chaining Mode - CBC
Decryption**



$$m_i = D_K(c_i) \oplus c_{i-1} \quad \text{for } i=1..N \quad c_0=IV$$

Notation:

M: 64-bit message block, with bits arranged as follows $M_1M_2\dots M_{64}$

C: 64-bit ciphertext block, with bits arranged as follows $C_1C_2\dots C_{64}$

X, Y: 64-bit intermediate variables

L(i), R(i): 32-bit intermediate variables

U: 48-bit intermediate variable

V(i): 6-bit intermediate variables

W(i): 4-bit intermediate variables

K(i): 48-bit round key $K(i)$

Operations:

$X \oplus Y$: bitwise XOR

$X \parallel Y$: X concatenated with Y

$IP(), IP^{-1}()$: fixed permutations

$Y=E(X)$: an expansion function replacing a 32-bit vector X with a 48-bit vector Y

$Y=Sbox(X)$: a 6x4 Sbox, i.e., a substitution function with a 6-bit input and a 4-bit output.

2. Table of input/output ports:

Port	Mode	Width	Function
clk	Input	1	System clock.
reset	Input	1	Asynchronous system reset.
s		1	Operating mode: 0 = loading round keys/ waiting for data, 1 = processing.
decrypt	Input	1	Control signal: decrypt=0 represents encryption, decrypt=1 represents decryption.
IV	Input	64	64-bit Initialization Vector.
write_IV	Input	1	Synchronous write control signal for the input IV.
Xi	Input	64	64-bit input block (message block M for encryption, ciphertext block C for decryption).
write_Xi	Input	1	Synchronous write control signal for the input Xi.
last_block	Input	1	Control signal indicating the last block of the message.
Kj	Input	48	Round key $K(j)$.
j	Input	4	Index of the round key $K(j)$, $j=0..15$.
write_Kj	Input	1	Synchronous write control signal for the round key $K(j)$.
done	Output	1	Control signal indicating that the output block is ready.
Yi	Output	64	64-bit output block (ciphertext block C for encryption, message block M for decryption) when $s=0$, high impedance otherwise.

3. Functional and timing requirements:

Assume that

- When $s=0$, round keys are loaded to the internal RAM. When $s=1$, the circuit is ready to perform encryption or decryption, depending on the values of control signals.
- Loading round keys to internal memory takes 16 clock cycles.

- Encryption of one message block takes 16 clock cycles.
- Decryption of one ciphertext block takes 16 clock cycles.

Tasks:

Task 1: Block Diagram [45 points]

Draw a block diagram of the datapath of the EXAM circuit using medium complexity components corresponding to the operations used in the pseudocode.

Your Datapath should

- be capable of executing the entire pseudocode given in point 1,
- match interface given in point 2, and
- meet all functional and timing requirements specified in point 3.

Clearly specify

- names, widths and directions of all buses
- names, widths and directions of all inputs and outputs of the logic components.

Minimize the number of control signals to be generated by the Control Unit.

Task 2: Substitution Sbox [5 points]

Explain in detail your implementation of the substitution function $Y=Sbox(X)$. Which logic component do you use to implement this function? How is this component initialized?

Task 3: Interface [10 points]

Draw an interface of the EXAM circuit, with the division into the Datapath and Controller. Show the names, widths, and directions of all signals forming this interface.

Problem 5 [bonus 10 points]

Write VHDL code describing the following functionality:

$$C = (A \ll 1) \oplus (A_{127} \cdot '8C9')$$

where

A and **C** are 128-bit buses,

A_{127} is the most significant bit of **A**,

'8C9' is a constant expressed in the hexadecimal representation,

$X \oplus Y$ is a bitwise XOR of vectors **X** and **Y**,

$x \cdot C$ is a multiplication of the binary variable **x** by the constant **C** (equal to **C** if $x=1$, and equal to 0 otherwise).