

ECE 545—Digital System Design with VHDL
Lecture 1A
 Digital Logic Refresher
 Part A – Combinational Logic Building Blocks

1

Lecture Roadmap – Combinational Logic

- Basic Logic Review
 - Basic Gates
 - De Morgan's Law
- Combinational Logic Building Blocks
 - Multiplexers
 - Decoders, Demultiplexers
 - Encoders, Priority Encoders
 - Arithmetic circuits
 - ROM. Implementing combinational logic using ROM.
 - Tri-state buffers.

2

Textbook References

- Combinational Logic Review
 - Stephen Brown and Zvonko Vranesic,
Fundamentals of Digital Logic with VHDL Design, 2nd or 3rd Edition
 - Chapter 2 Introduction to Logic Circuits (2.1-2.8 only)
 - Chapter 6 Combinational-Circuit Building Blocks (6.1-6.5 only)
 - **OR** your undergraduate digital logic textbook (chapters on combinational logic)

3

Basic Logic Review

some slides modified from:
 S. Dandamudi, "Fundamentals of Computer Organization and Design"


4

Rules


- If you believe that you know a correct answer, please raise your hand
- I will select *one or more* students (independently whether an answer given by the first student is correct or incorrect)
- Please, identify yourself by first name and give an answer
- **Correct answer = 1 bonus point**

5


Basic Logic Gates (2-input versions)




AND

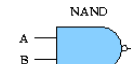


NAND

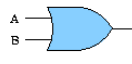


OR

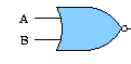

NOR



XOR



XNOR

A	B	AND	OR	XOR	NAND	NOR	XNOR
0	0	0	0	0	1	1	1
0	1	0	1	1	1	0	0
1	0	0	1	1	1	0	0
1	1	1	1	0	0	0	1

6

Basic Logic Gates Generalized

- Simple logic gates
 - AND \rightarrow 0 if one or more inputs is 0
 - OR \rightarrow 1 if one or more inputs is 1
 - NAND = AND + NOT
 - 1 if one or more inputs is 0
 - NOR = OR + NOT
 - 0 if one or more input is 1
 - XOR \rightarrow 1 if an odd number of inputs is 1
 - XNOR \rightarrow 1 if an even number of inputs is 1
 - NAND and NOR gates require fewer transistors than AND and OR in standard CMOS
- Functionality can be expressed by a truth table
 - A truth table lists output for each possible input combination

7

Number of Functions

- Number of functions
 - With N logical variables, we can define 2^{2^N} functions
 - Some of them are useful
 - AND, NAND, NOR, XOR, ...
 - Some are not useful:
 - Output is always 1
 - Output is always 0
 - “Number of functions” definition is useful in proving completeness property

8


Complete Set of Gates

- Complete sets
 - A set of gates is complete
 - if we can implement any logic function using only the type of gates in the set
 - Some example complete sets
 - {AND, OR, NOT} \leftarrow Not a minimal complete set
 - {AND, NOT}
 - {OR, NOT}
 - {NAND}
 - {NOR}
 - Minimal complete set
 - A complete set with no redundant elements.

9

NAND as a Complete Set

- Proving NAND gate is universal

 

10

Logic Functions

- Logic functions can be expressed in several ways:
 - Truth table
 - Logical expressions
 - Graphical schematic form
 - HDL code
- Example:
 - Majority function
 - Output is one whenever majority of inputs is 1
 - We use 3-input majority function

11

Alternative Representations of Logic Function


Truth table

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Logical expression form

$$F = A B + B C + A C$$

Graphical schematic form

 

HDL code: $F <= (A \text{ AND } B) \text{ OR } (B \text{ AND } C) \text{ OR } (A \text{ AND } C);$

12

Boolean Algebra

Boolean identities		
Name	AND version	OR version
Identity	$x \cdot 1 = x$	$x + 0 = x$
Complement	$x \cdot x' = 0$	$x + x' = 1$
Commutative	$x \cdot y = y \cdot x$	$x + y = y + x$
Distribution	$x \cdot (y + z) = xy + xz$	$x + (y \cdot z) = (x + y)(x + z)$
Idempotent	$x \cdot x = x$	$x + x = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$

13

Boolean Algebra (cont' d)


- Boolean identities (cont' d)

Name	AND version	OR version
Involution	$x = (x')'$	---
Absorption	$x \cdot (x + y) = x$	$x + (x \cdot y) = x$
Associative	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) = (x + y) + z$
de Morgan	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$

(de Morgan's law in particular is very useful)

14

Alternative symbols for NAND and NOR

 

15

Deriving Equivalent Expressions

- Using NAND gates
 - Get an equivalent expression

$$A B + C D = (A B + C D)'$$
 - Using de Morgan's law


$$A B + C D = ((A B)' \cdot (C D)')'$$
- Can be generalized
 - Example: Majority function

$$A B + B C + A C = ((A B)' \cdot (B C)' \cdot (A C)')'$$

16

Majority Function Using Other Gates

- Majority function

 


17

Combinational Logic Building Blocks

Some slides modified from:
S. Dandamudi, "Fundamentals of Computer Organization and Design"
S. Brown and Z. Vranesic, "Fundamentals of Digital Logic"

18

Multiplexers

 

- multiplexer
 - n binary inputs (binary input = 1-bit input)
 - $\log_2 n$ binary selection inputs
 - 1 binary output
 - Function: one of n inputs is placed onto output
 - Called **n-to-1** multiplexer

19



2-to-1 Multiplexer



s	f
0	w_0
1	w_1

(a) Graphical symbol

(b) Truth table

  

(c) Sum-of-products circuit

(d) Circuit with transmission gates

Source: Brown and Vranesic

20


4-to-1 Multiplexer



s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

(a) Graphical symbol

(b) Truth table

 

(c) Circuit

Source: Brown and Vranesic

21

Multi-bit 4-to-1 Multiplexer



s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3


(a) Graphical symbol

(b) Truth table

- When drawing schematics, can draw **multi-bit** multiplexers
- Example: 8-bit 4-to-1 multiplexer
 - 4 inputs (each 8 bits)
 - 1 output (8 bits)
 - 2 selection bits
- Can also have multi-bit 2-to-1 muxes, 16-to-1 muxes, etc.

22


8-bit 4-to-1 Multiplexer

 

An 8-bit 4-to-1 multiplexer is composed of eight [1-bit] 4-to-1 multiplexers

23

Decoders

 

- Decoder
 - n binary inputs
 - 2^n binary outputs
 - Function: decode encoded information
 - If enable=1, one output is asserted high, the other outputs are asserted low
 - If enable=0, all outputs asserted low
 - Often, enable pin is not needed (i.e. the decoder is always enabled)
 - Called **n-to-2ⁿ** decoder
 - Can consider n binary inputs as a single n -bit input
 - Can consider 2^n binary outputs as a single 2^n -bit output
 - Decoders are often used for RAM/ROM addressing


24

2-to-4 Decoder

E_n	w_1	w_0	y_3	y_2	y_1	y_0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	-	-	0	0	0	0

(a) Truth table

(b) Graphical symbol

 

(c) Logic circuit

Source: Brown and Vranesic


25

Problem 8

Show how to implement a decoder that recognizes the following 4 ranges of a 16-bit address A, and generates the corresponding enable signals e_0, e_1, e_2, e_3 :

For A in:	Assert
C000-CFFF:	e_0
D000-DFFF:	e_1
E000-EFFF:	e_2
F000-FFFF:	e_3


Demultiplexers

 

- Demultiplexer
 - 1 binary input
 - n binary outputs
 - $\log_2 n$ binary selection inputs
 - Function: places input onto one of n outputs, with the remaining outputs asserted low
 - Called **1-to-n** demultiplexer
- Closely related to decoder
 - Can build 1-to-n demultiplexer from $\log_2 n$ -to-n decoder by using the decoder's enable signal as the demultiplexer's input signal, and using decoder's input signals as the demultiplexer's selection input signals.


27

1-to-4 Demultiplexer

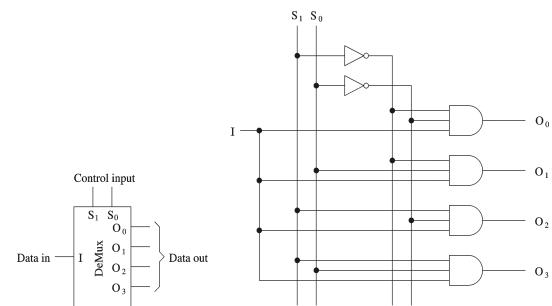

28

Encoders

 


- Encoder
 - 2^n binary inputs
 - n binary outputs
 - Function: encodes information into an n-bit code
 - Called **2^n -to-n** encoder
 - Can consider 2^n binary inputs as a single 2^n -bit input
 - Can consider n binary output as a single n-bit output
- Encoders only work when **exactly one** binary input is equal to 1

29

4-to-2 Encoder

w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1


(a) Truth table

 

(b) Circuit

30

Priority Encoders

 

- Priority Encoder
 - 2^n binary inputs
 - n binary outputs
 - 1 binary "valid" output
 - Function: encodes information into an n-bit code based on priority of inputs
 - Called 2^n -to-n priority encoder
- Priority encoder allows for multiple inputs to have a value of '1', as it encodes the input with the highest priority (MSB = highest priority, LSB = lowest priority)
 - "valid" output indicates when priority encoder output is valid
 - Priority encoder is more common than an encoder


31

4-to-2 MSB Priority Encoder

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	-	-	0
0	0	0	1	0	0	1
0	0	1	-	0	1	1
0	1	-	-	1	0	1
1	-	-	-	1	1	1


32

4x4-bit Unsigned Multiplier

 

33

4x4-bit Signed Multiplier

 


34

Unsigned vs. Signed Multiplication

Unsigned		Signed	
1111	15	1111	-1
x 1111	x 15	x 1111	x -1
<hr/>		<hr/>	
11100001	225	00000001	1


35

Logical Shift Right

 


36

Arithmetic Shift Right

 


37

Fixed Rotation

 


38

8-bit Variable Rotator Left

 


39

Read Only Memory (ROM)

 


40

 Implementing Arbitrary Combinational Logic Using ROM




41

Tri-state Buffer

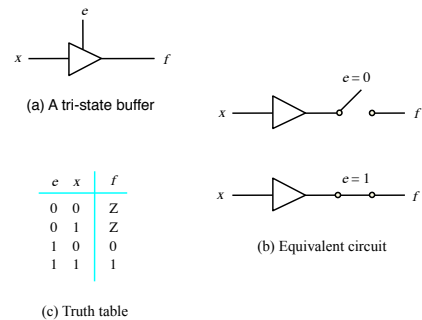


42


Four types of Tri-state Buffers

 


(a)

 

(b)

 

(c)

 

(d)