

Lecture 7

Tree and Array Multipliers

Required Reading

Behrooz Parhami,

Computer Arithmetic: Algorithms and Hardware Design

Chapter 11, Tree and Array Multipliers

Chapter 12.5, The special case of squaring

Note errata at:

http://www.ece.ucsb.edu/~parhami/text_comp_arit_1ed.htm#errors

“At least one good reason for studying multiplication and division is that there is an infinite number of ways of performing these operations and hence there is an infinite number of PhDs (or expenses-paid visits to conferences in the USA) to be won from inventing new forms of multiplier.”


Alan Clements

The Principles of Computer Hardware, 1986

Notation

a	Multiplicand	$a_{k-1} a_{k-2} \dots a_1 a_0$
x	Multiplier	$x_{k-1} x_{k-2} \dots x_1 x_0$
p	Product (a · x)	$p_{2k-1} p_{2k-2} \dots p_2 p_1 p_0$

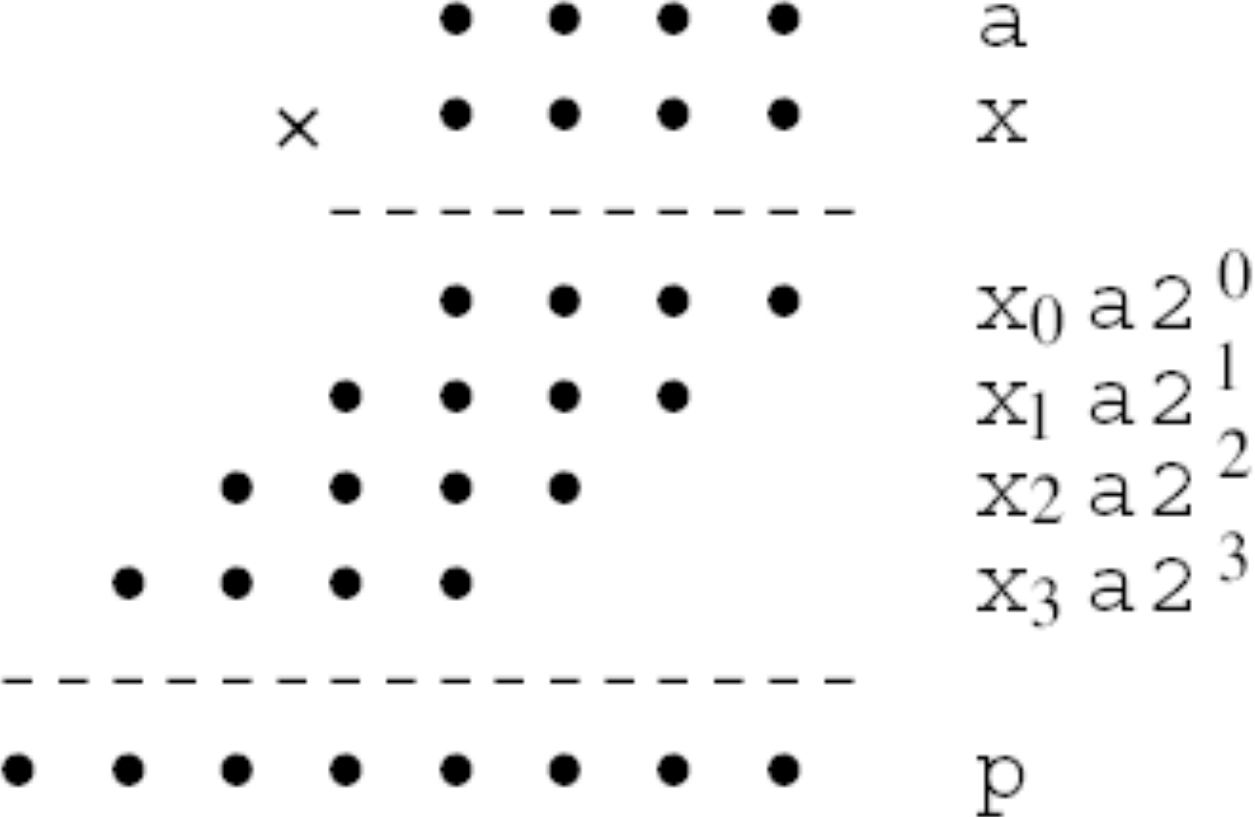Multiplication of two 4-bit unsigned binary numbers in dot notation



Basic Multiplication Equations


$$p = a \cdot x \qquad x = \sum_{i=0}^{k-1} x_i \cdot 2^i$$

$$\begin{aligned} p = a \cdot x &= \sum_{i=0}^{k-1} a \cdot x_i \cdot 2^i = \\ &= x_0 a 2^0 + x_1 a 2^1 + x_2 a 2^2 + \dots + x_{k-1} a 2^{k-1} \end{aligned}$$


Unsigned Multiplication

					a_4	a_3	a_2	a_1	a_0
				x	x_4	x_3	x_2	x_1	x_0
ax_0	2^0				a_4x_0	a_3x_0	a_2x_0	a_1x_0	a_0x_0
ax_1	2^1	+			a_4x_1	a_3x_1	a_2x_1	a_1x_1	a_0x_1
ax_2	2^2				a_4x_2	a_3x_2	a_2x_2	a_1x_2	a_0x_2
ax_3	2^3				a_4x_3	a_3x_3	a_2x_3	a_1x_3	a_0x_3
ax_4	2^4				a_4x_4	a_3x_4	a_2x_4	a_1x_4	a_0x_4
		p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2
								p_1	p_0


Full tree multiplier - general structure

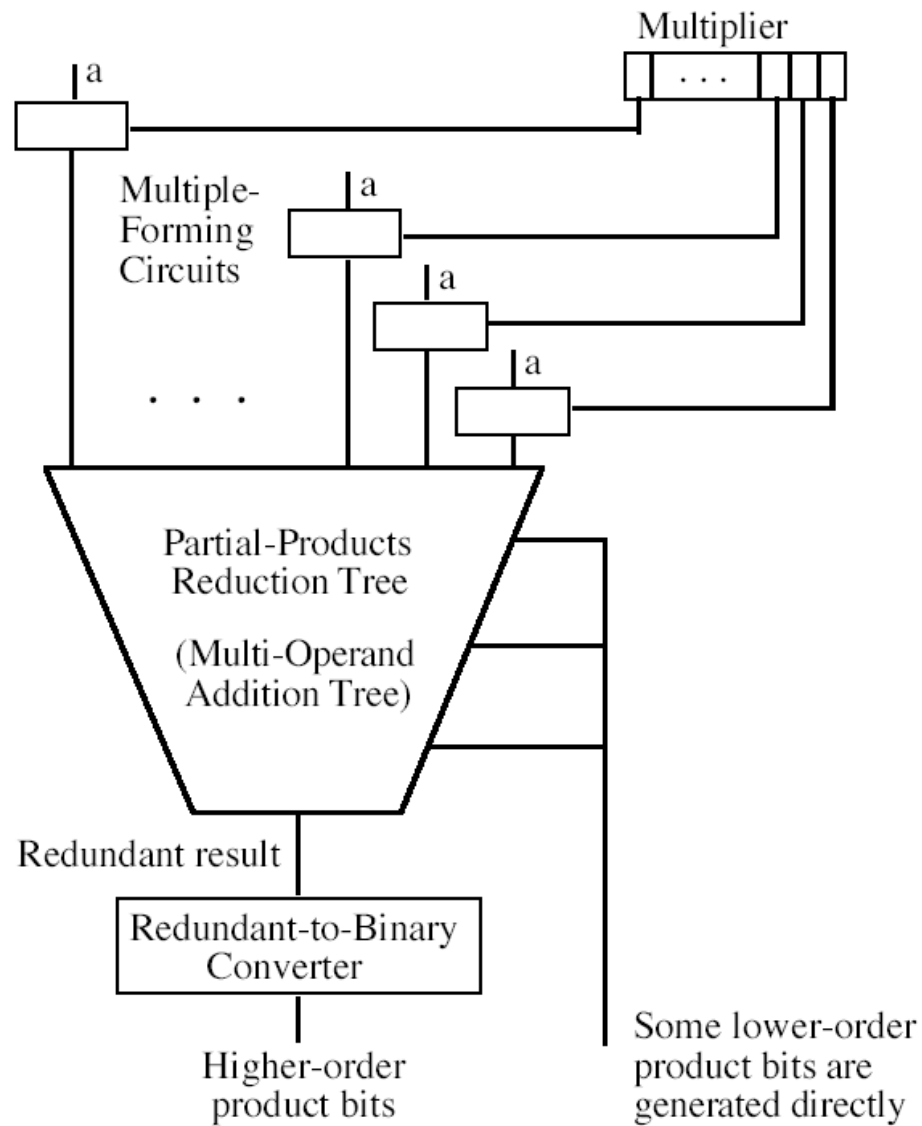


7 x 7 tree multiplier

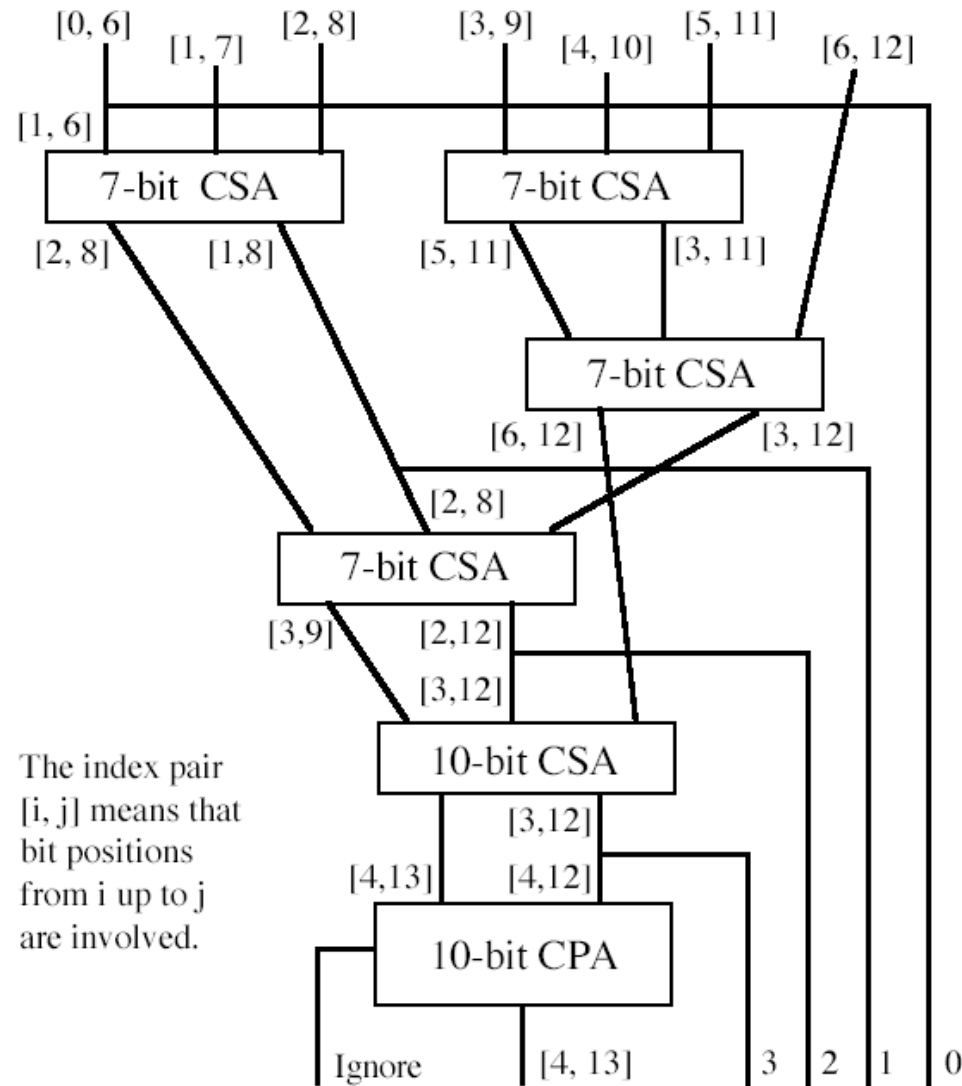

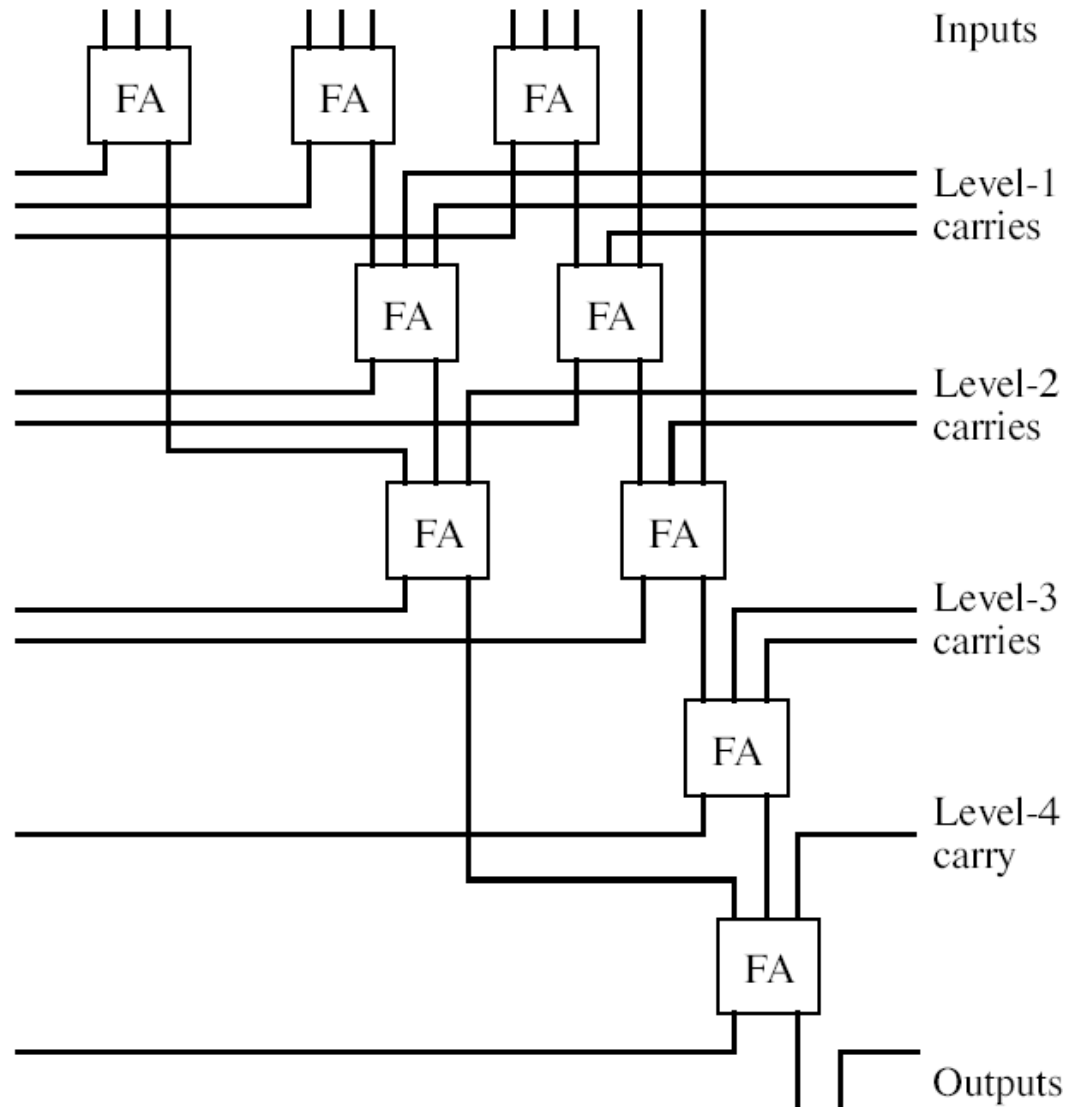
A slice of a balanced-delay tree for 11 inputs



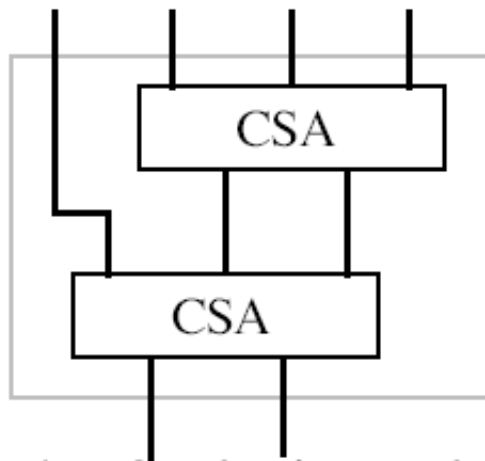Tree multiplier with a more regular structure



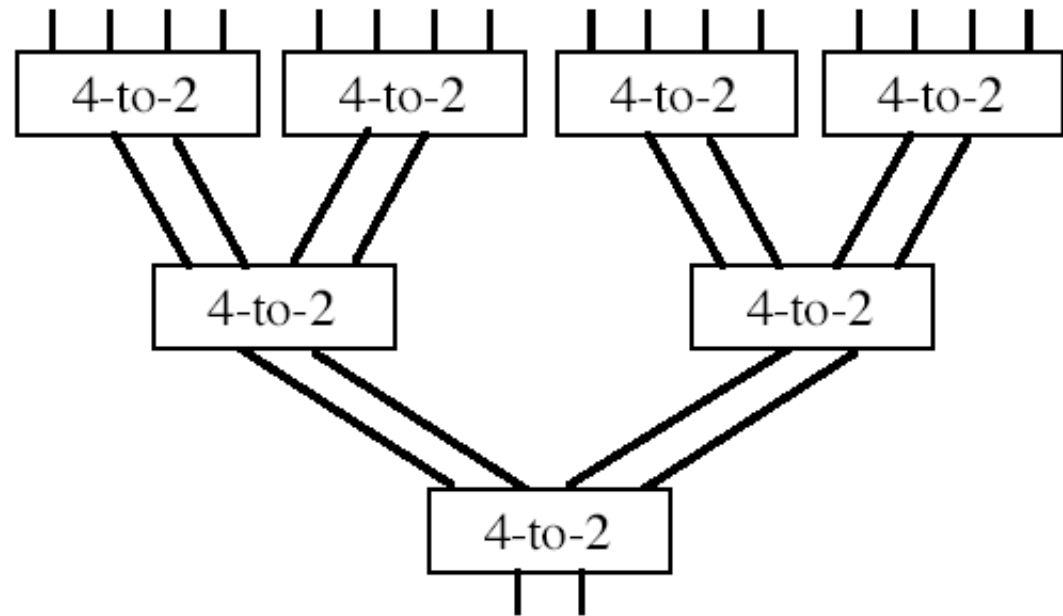4-to-2 reduction module
implemented with two
levels of (3; 2)-counters



Unsigned vs. Signed Multiplication

Unsigned


1111	15
x 1111	x 15
<hr/>	
11100001	225

Signed

1111	-1
x 1111	x -1
<hr/>	
00000001	1

2' s Complement Multiplication (1)

	-2^4	2^3	2^2	2^1	2^0
	\mathbf{a}_4	a_3	a_2	a_1	a_0
x	\mathbf{x}_4	x_3	x_2	x_1	x_0

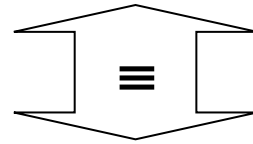


	2^4	2^3	2^2	2^1	2^0
	$-\mathbf{a}_4$	a_3	a_2	a_1	a_0
x	$-\mathbf{x}_4$	x_3	x_2	x_1	x_0

2' s Complement Multiplication (2)

				$-a_4$	a_3	a_2	a_1	a_0		
			x	$-x_4$	x_3	x_2	x_1	x_0		
				$-a_4x_0$	a_3x_0	a_2x_0	a_1x_0	a_0x_0		
	+			$-a_4x_1$	a_3x_1	a_2x_1	a_1x_1	a_0x_1		
				$-a_4x_2$	a_3x_2	a_2x_2	a_1x_2	a_0x_2		
				$-a_4x_3$	a_3x_3	a_2x_3	a_1x_3	a_0x_3		
			a_4x_4	$-a_3x_4$	$-a_2x_4$	$-a_1x_4$	$-a_0x_4$			
-p₉	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	
2⁹	2^8	2^7	2^6	2^5	2^4	2^3	2^2	2^1	2^0	

2' s Complement Multiplication (3)

-P₉	P ₈	P ₇	P ₆	P ₅	P ₄	P ₃	P ₂	P ₁	P ₀
2⁹	2 ⁸	2 ⁷	2 ⁶	2 ⁵	2 ⁴	2 ³	2 ²	2 ¹	2 ⁰

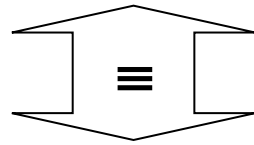

P₉	P ₈	P ₇	P ₆	P ₅	P ₄	P ₃	P ₂	P ₁	P ₀
-2⁹	2 ⁸	2 ⁷	2 ⁶	2 ⁵	2 ⁴	2 ³	2 ²	2 ¹	2 ⁰

2' s Complement Multiplication (4)

$$\bar{z} = 1 - z$$

$$z = 1 - \bar{z}$$

$$-a_j x_i = -a_j (1 - \bar{x}_i) = a_j \bar{x}_i - a_j = a_j \bar{x}_i + a_j - 2 a_j$$

$$-a_j x_i = -(1 - \bar{a}_j) x_i = \bar{a}_j x_i - x_i = \bar{a}_j x_i + x_i - 2 x_i$$

$$-a_j x_i = -(1 - \overline{a_j x_i}) = \overline{a_j x_i} - 1 = \overline{a_j x_i} + 1 - 2$$

$$-a_j = -(1 - \bar{a}_j) = \bar{a}_j - 1 = \bar{a}_j + 1 - 2$$


$$-x_i = -(1 - \bar{x}_i) = \bar{x}_i - 1 = \bar{x}_i + 1 - 2$$

$$\begin{aligned}
 & -a_4 x_0 \\
 & -a_4 x_1 \\
 & -a_4 x_2 \\
 + & -a_4 x_3
 \end{aligned}$$

$$\begin{array}{cccc}
 & & & -a_4 \quad a_4 \overline{x_0} \\
 & & & \phantom{a_4 \overline{x_0}} \\
 & & -a_4 \quad a_4 \overline{x_1} & a_4 \\
 & & \phantom{a_4 \overline{x_1}} & \\
 & -a_4 \quad a_4 \overline{x_2} & a_4 & \\
 & \phantom{a_4 \overline{x_2}} & & \\
 -a_4 \quad a_4 \overline{x_3} & a_4 & & \\
 \phantom{a_4 \overline{x_3}} & & & \\
 & a_4 & & \\
 & & &
 \end{array}$$

$$\begin{array}{ccccccc}
 \overline{a_4} & \overline{a_4 x_3} & \overline{a_4 x_2} & \overline{a_4 x_1} & \overline{a_4 x_0} & & \\
 -1 & & & & a_4 & &
 \end{array}$$
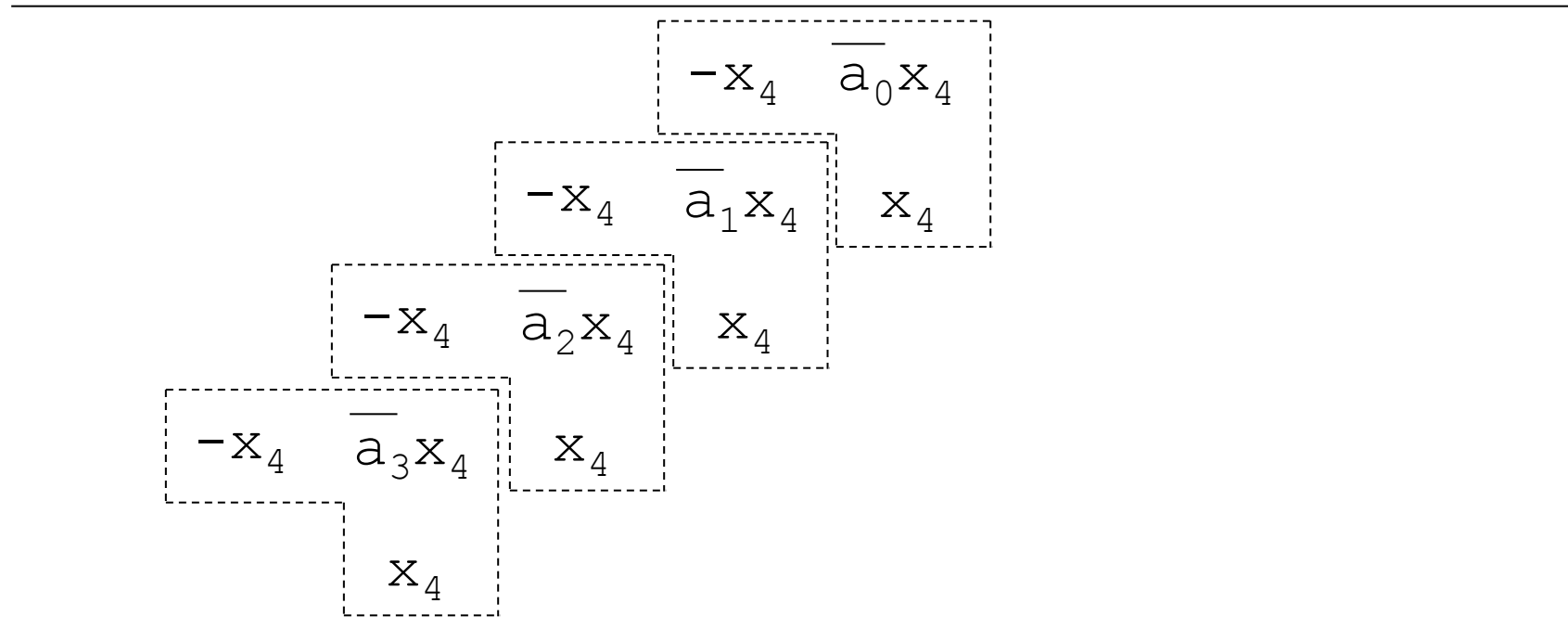
$$+ \quad -a_3x_4 \quad -a_2x_4 \quad -a_1x_4 \quad -a_0x_4$$



$$\overline{x_4} \quad \overline{a_3}x_4 \quad \overline{a_2}x_4 \quad \overline{a_1}x_4 \quad \overline{a_0}x_4$$


$$-1 \quad \quad \quad \quad \quad x_4$$

2^9 2^8 2^7 2^6 2^5 2^4 $\overline{a_4}$ $\overline{a_4 x_3}$ $\overline{a_4 x_2}$ $\overline{a_4 x_1}$ $\overline{a_4 x_0}$ -1 a_4 $\overline{x_4}$ $\overline{a_3 x_4}$ $\overline{a_2 x_4}$ $\overline{a_1 x_4}$ $\overline{a_0 x_4}$ -1 x_4 -1 $\overline{a_4}$ $\overline{a_4 x_3}$ $\overline{a_4 x_2}$ $\overline{a_4 x_1}$ $\overline{a_4 x_0}$ $\overline{x_4}$ $\overline{a_3 x_4}$ $\overline{a_2 x_4}$ $\overline{a_1 x_4}$ $\overline{a_0 x_4}$ a_4 x_4 1 $\overline{a_4}$ $\overline{a_4 x_3}$ $\overline{a_4 x_2}$ $\overline{a_4 x_1}$ $\overline{a_4 x_0}$ $\overline{x_4}$ $\overline{a_3 x_4}$ $\overline{a_2 x_4}$ $\overline{a_1 x_4}$ $\overline{a_0 x_4}$ a_4 x_4 -2^9


Baugh-Wooley 2's Complement Multiplier

$$\begin{array}{rcccccccc}
 & & & & & -a_4 & a_3 & a_2 & a_1 & a_0 \\
 x & & & & & -x_4 & x_3 & x_2 & x_1 & x_0 \\
 \hline
 & & & & & \overline{a_4 x_0} & a_3 x_0 & a_2 x_0 & a_1 x_0 & a_0 x_0 \\
 & & & & + & \overline{a_4 x_1} & a_3 x_1 & a_2 x_1 & a_1 x_1 & a_0 x_1 \\
 & & & & & \overline{a_4 x_2} & a_3 x_2 & a_2 x_2 & a_1 x_2 & a_0 x_2 \\
 & & & & & \overline{a_4 x_3} & a_3 x_3 & a_2 x_3 & a_1 x_3 & a_0 x_3 \\
 & & & & & \overline{a_4 x_4} & \overline{a_3 x_4} & \overline{a_2 x_4} & \overline{a_1 x_4} & \overline{a_0 x_4} \\
 & & & & & \overline{a_4} & & & & & a_4 \\
 & & & & & \overline{x_4} & & & & & x_4 \\
 \hline
 \mathbf{P_9} & p_8 & p_7 & p_6 & p_5 & p_4 & p_3 & p_2 & p_1 & p_0 \\
 \mathbf{-2^9} & 2^8 & 2^7 & 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0
 \end{array}$$
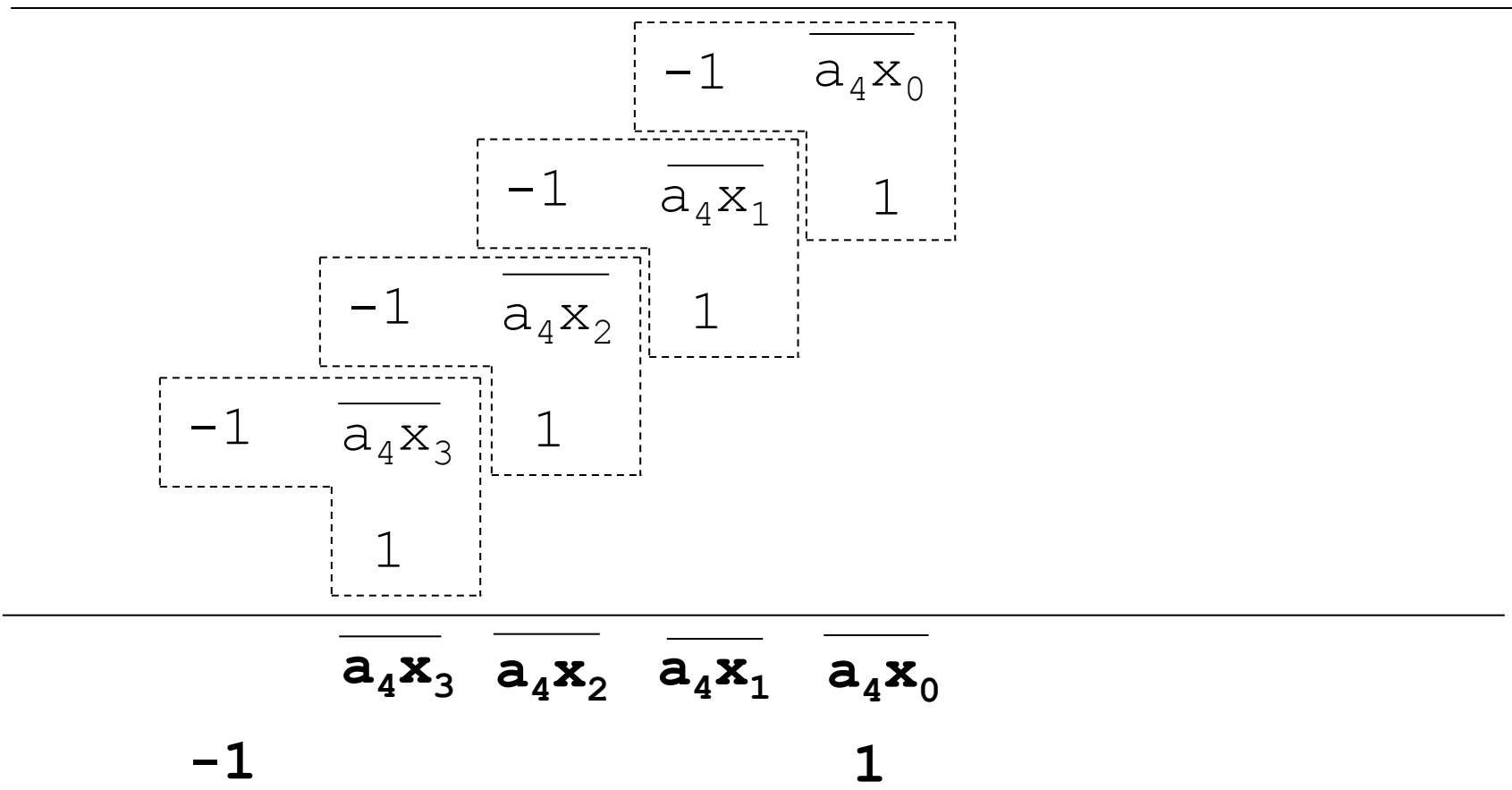
$$\begin{aligned}
 & -a_4x_0 \\
 & -a_4x_1 \\
 & -a_4x_2 \\
 + & -a_4x_3
 \end{aligned}$$


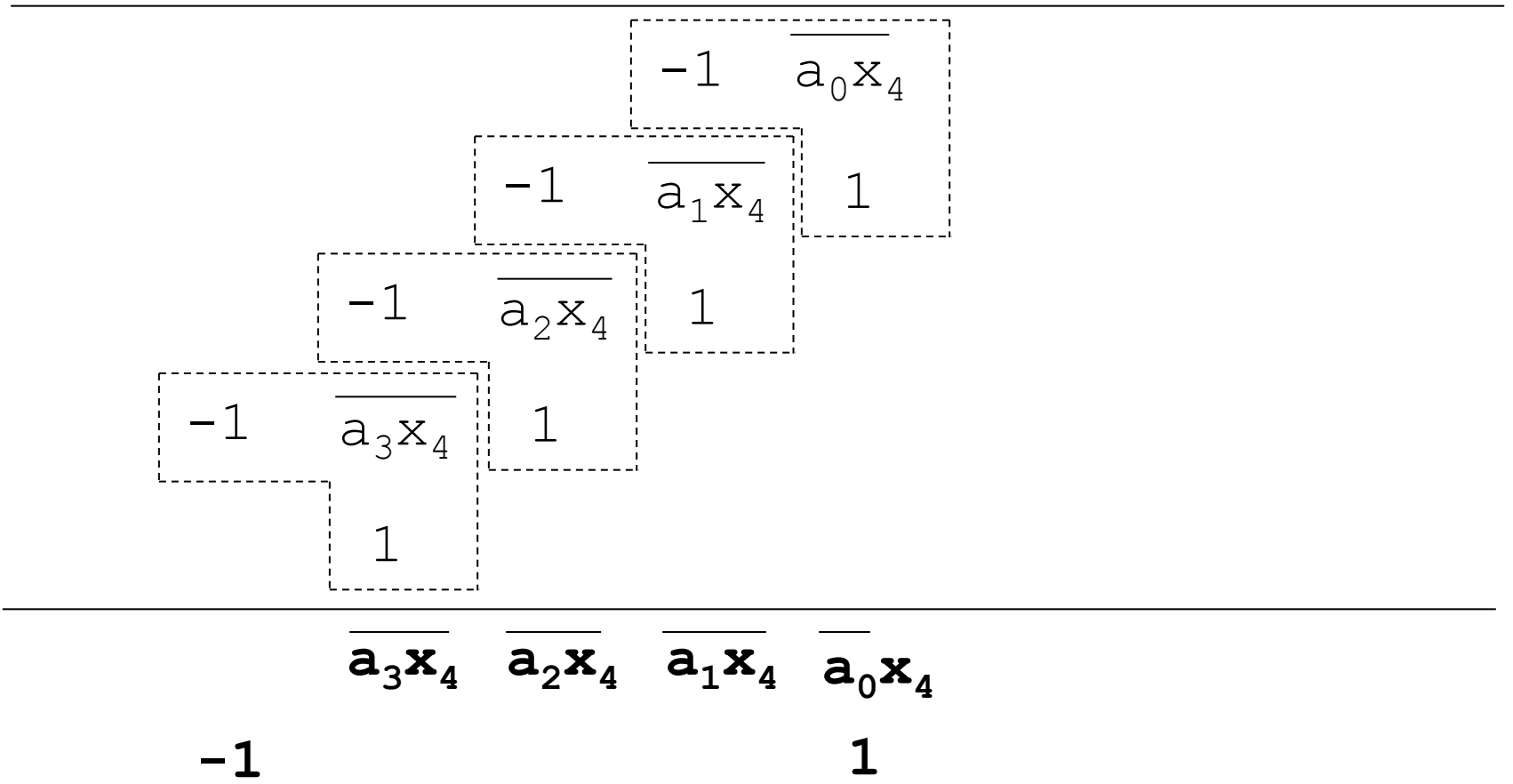
$$+ \quad -a_3x_4 \quad -a_2x_4 \quad -a_1x_4 \quad -a_0x_4$$



$$\boxed{2^9}$$

$$\begin{array}{rcccccc} 2^8 & 2^7 & 2^6 & 2^5 & 2^4 & \\ & \overline{a_4 x_3} & \overline{a_4 x_2} & \overline{a_4 x_1} & \overline{a_4 x_0} & \\ -1 & & & & 1 & \\ & \overline{a_3 x_4} & \overline{a_2 x_4} & \overline{a_1 x_4} & \overline{a_0 x_4} & \\ -1 & & & & 1 & \end{array}$$

$$\begin{array}{rcccccc} & \overline{a_4 x_3} & \overline{a_4 x_2} & \overline{a_4 x_1} & \overline{a_4 x_0} & \\ & \overline{a_3 x_4} & \overline{a_2 x_4} & \overline{a_1 x_4} & \overline{a_0 x_4} & \\ -1 & & & 1 & & \end{array}$$


$$\begin{array}{rcccccc} & \overline{a_4 x_3} & \overline{a_4 x_2} & \overline{a_4 x_1} & \overline{a_4 x_0} & \\ & \overline{a_3 x_4} & \overline{a_2 x_4} & \overline{a_1 x_4} & \overline{a_0 x_4} & \\ 1 & & & 1 & & \end{array}$$

$$\boxed{-2^9}$$


Modified Baugh-Wooley Multiplier

$$\begin{array}{r}
 \begin{array}{cccccc}
 & & & & -a_4 & a_3 & a_2 & a_1 & a_0 \\
 x & & & & -x_4 & x_3 & x_2 & x_1 & x_0 \\
 \hline
 & & & & \overline{a_4 x_0} & a_3 x_0 & a_2 x_0 & a_1 x_0 & a_0 x_0 \\
 + & & & & \overline{a_4 x_1} & a_3 x_1 & a_2 x_1 & a_1 x_1 & a_0 x_1 \\
 & & & & \overline{a_4 x_2} & a_3 x_2 & a_2 x_2 & a_1 x_2 & a_0 x_2 \\
 & & & & \overline{a_4 x_3} & a_3 x_3 & a_2 x_3 & a_1 x_3 & a_0 x_3 \\
 & a_4 x_4 & \overline{a_3 x_4} & \overline{a_2 x_4} & \overline{a_1 x_4} & \overline{a_0 x_4} & & & & \\
 1 & & & & 1 & & & & & \\
 \hline
 \mathbf{p_9} & p_8 & p_7 & p_6 & p_5 & p_4 & p_3 & p_2 & p_1 & p_0 \\
 \mathbf{-2^9} & 2^8 & 2^7 & 2^6 & 2^5 & 2^4 & 2^3 & 2^2 & 2^1 & 2^0
 \end{array}
 \end{array}$$


Basic array multiplier

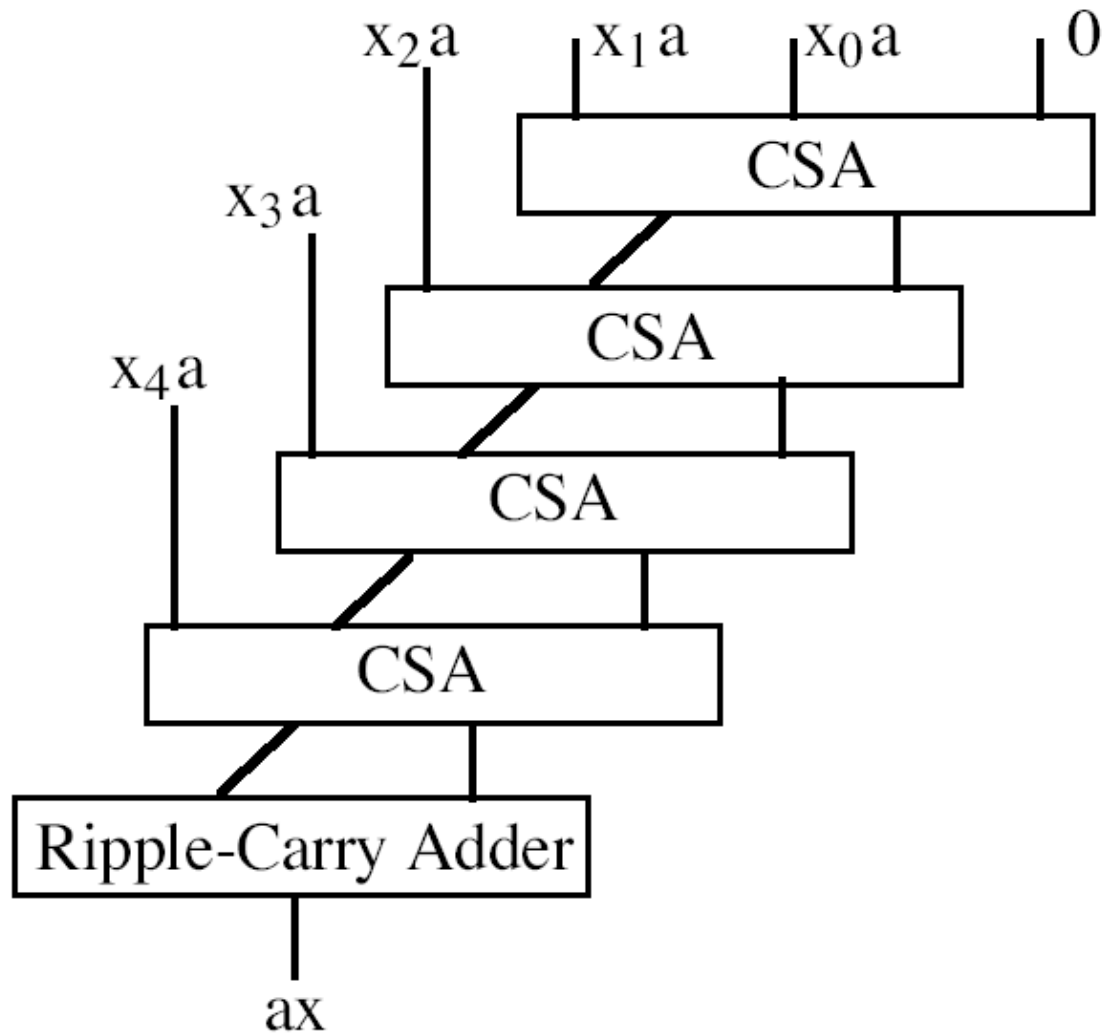


5 x 5 Array Multiplier

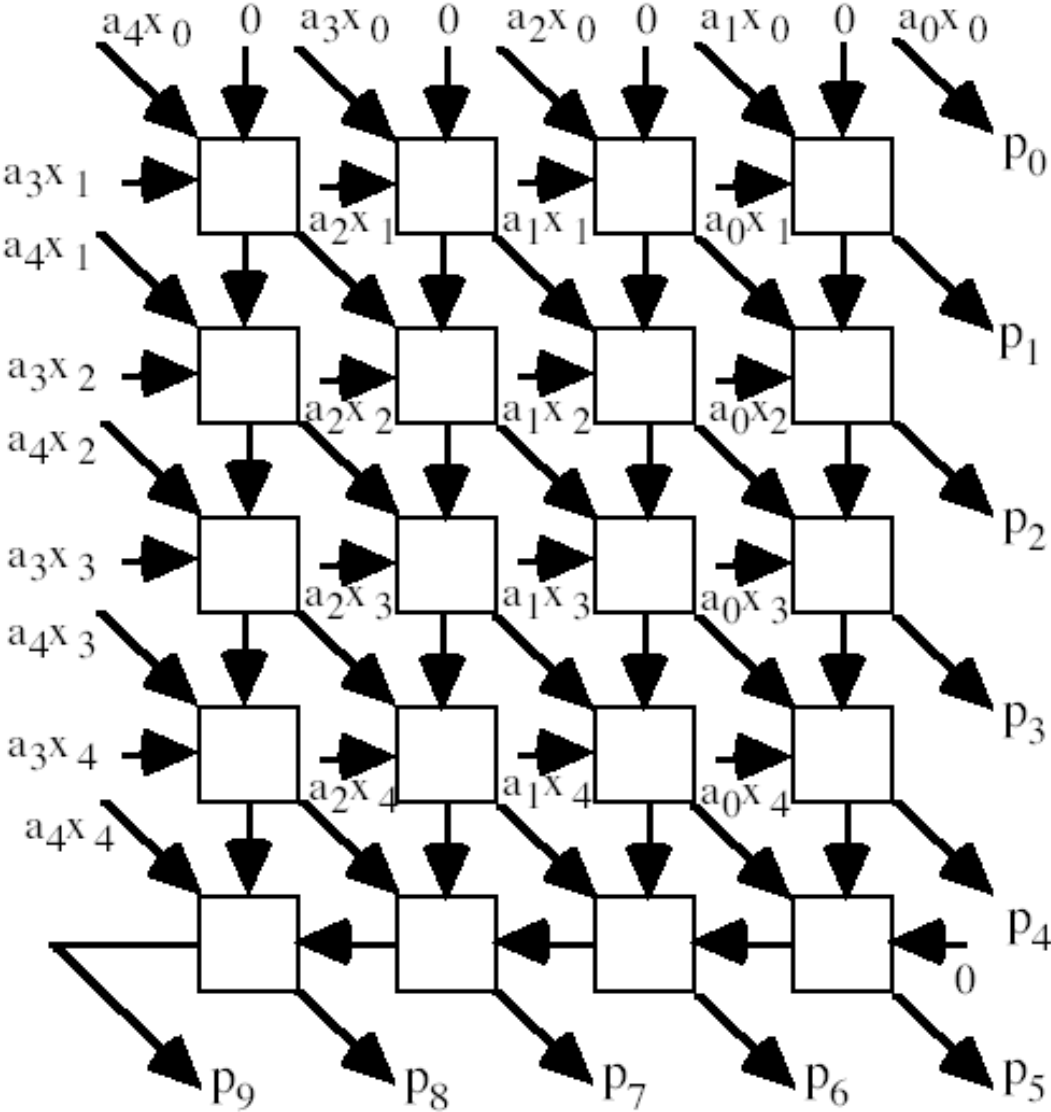


Array Multiplier - Basic Cell

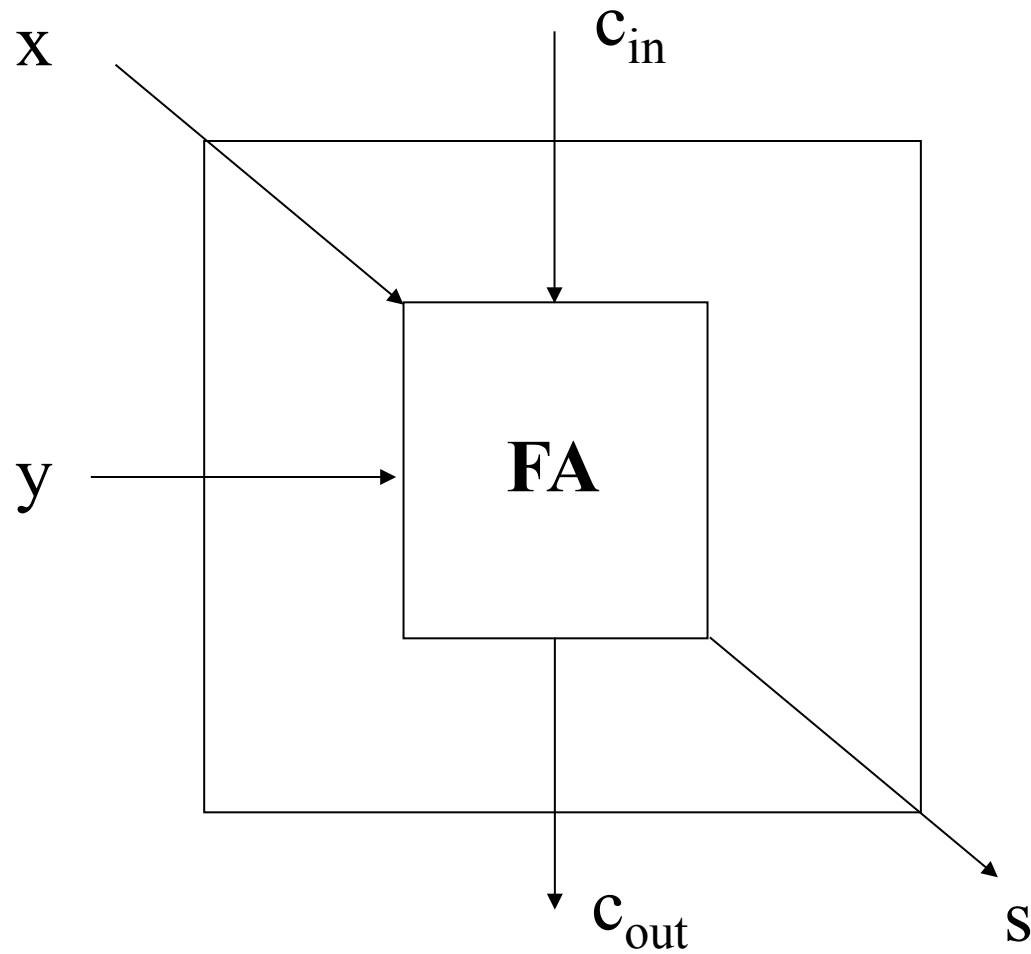


Modifications in a 5 x 5 multiplier

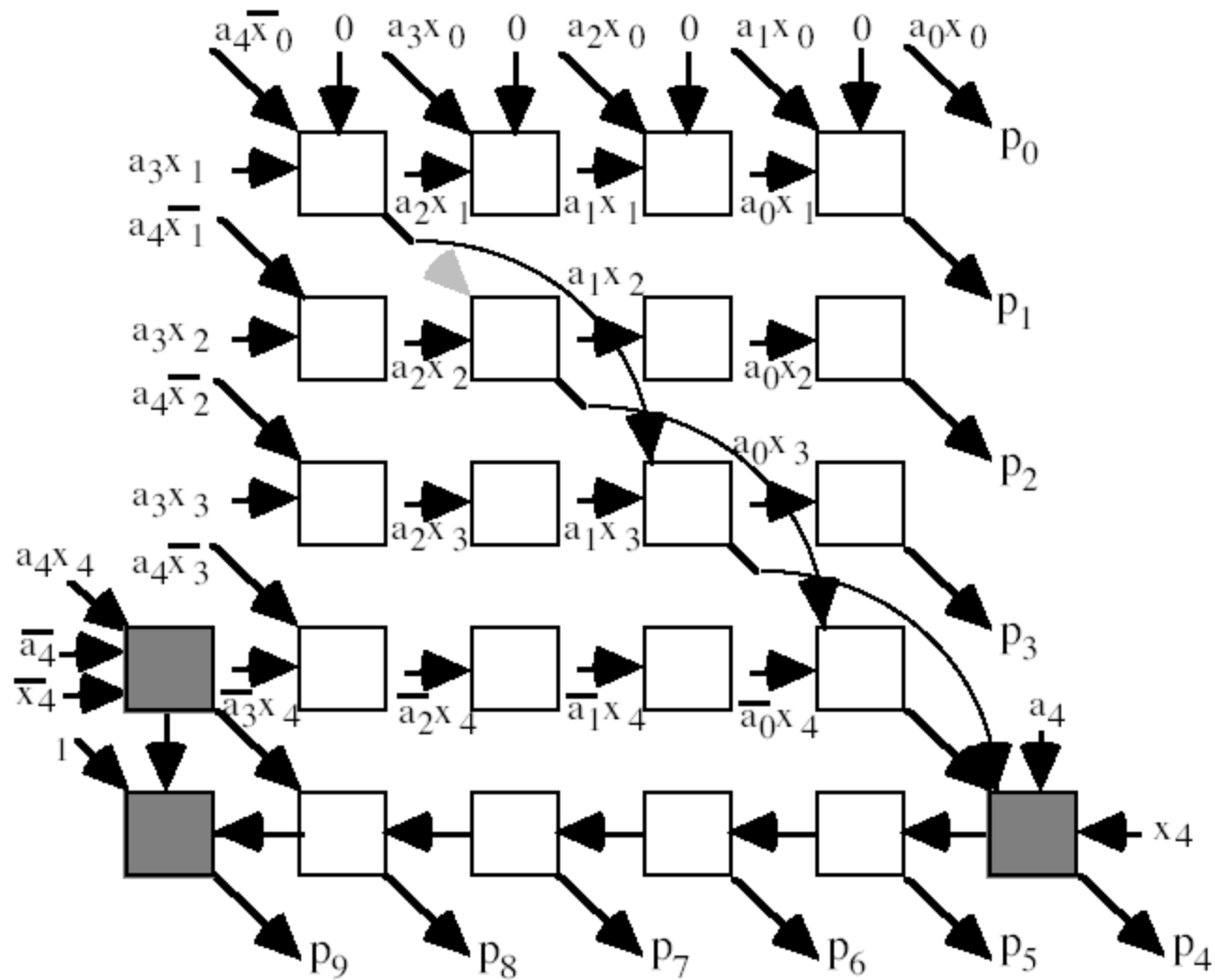


Array Multiplier – Modified Basic Cell

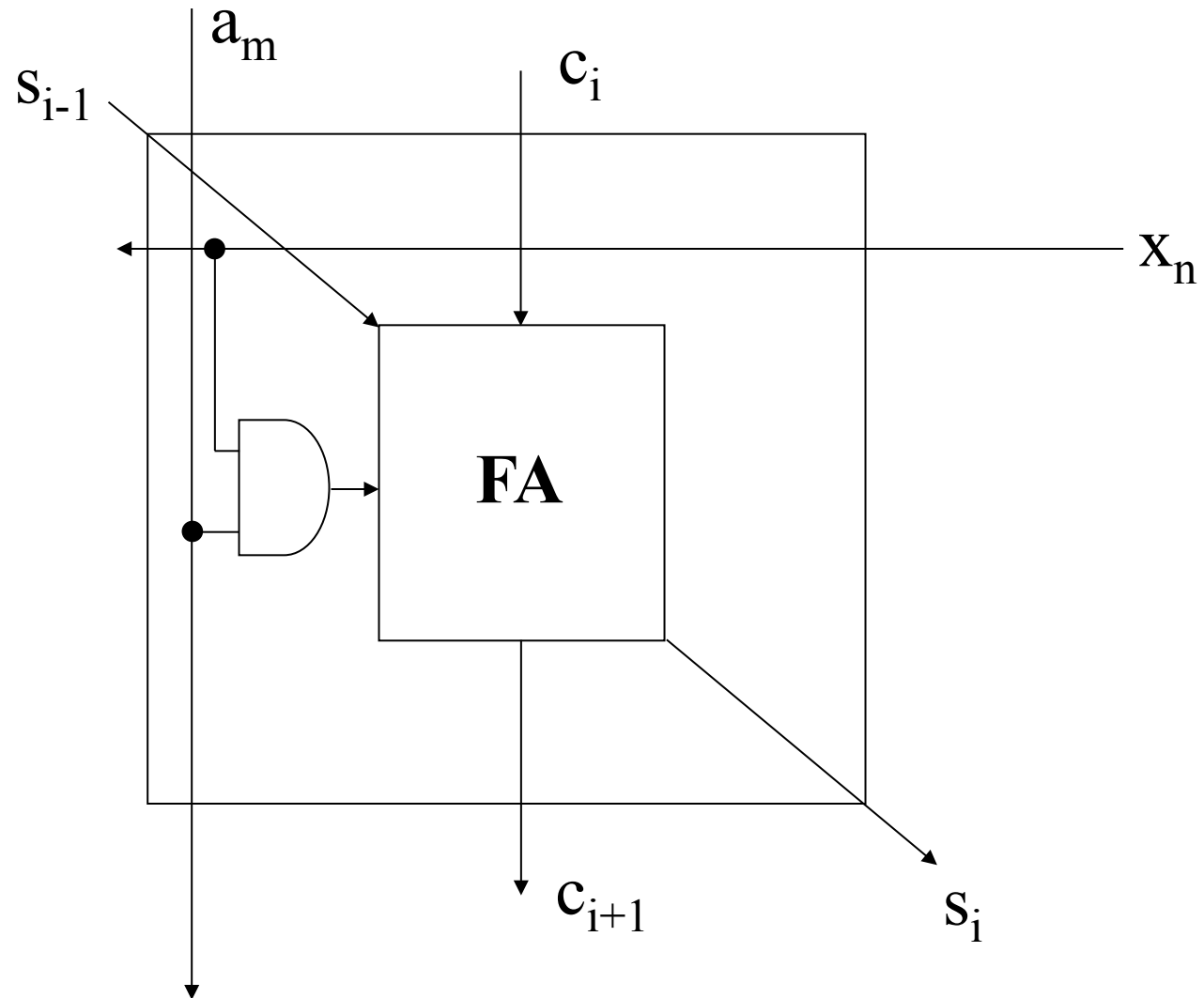

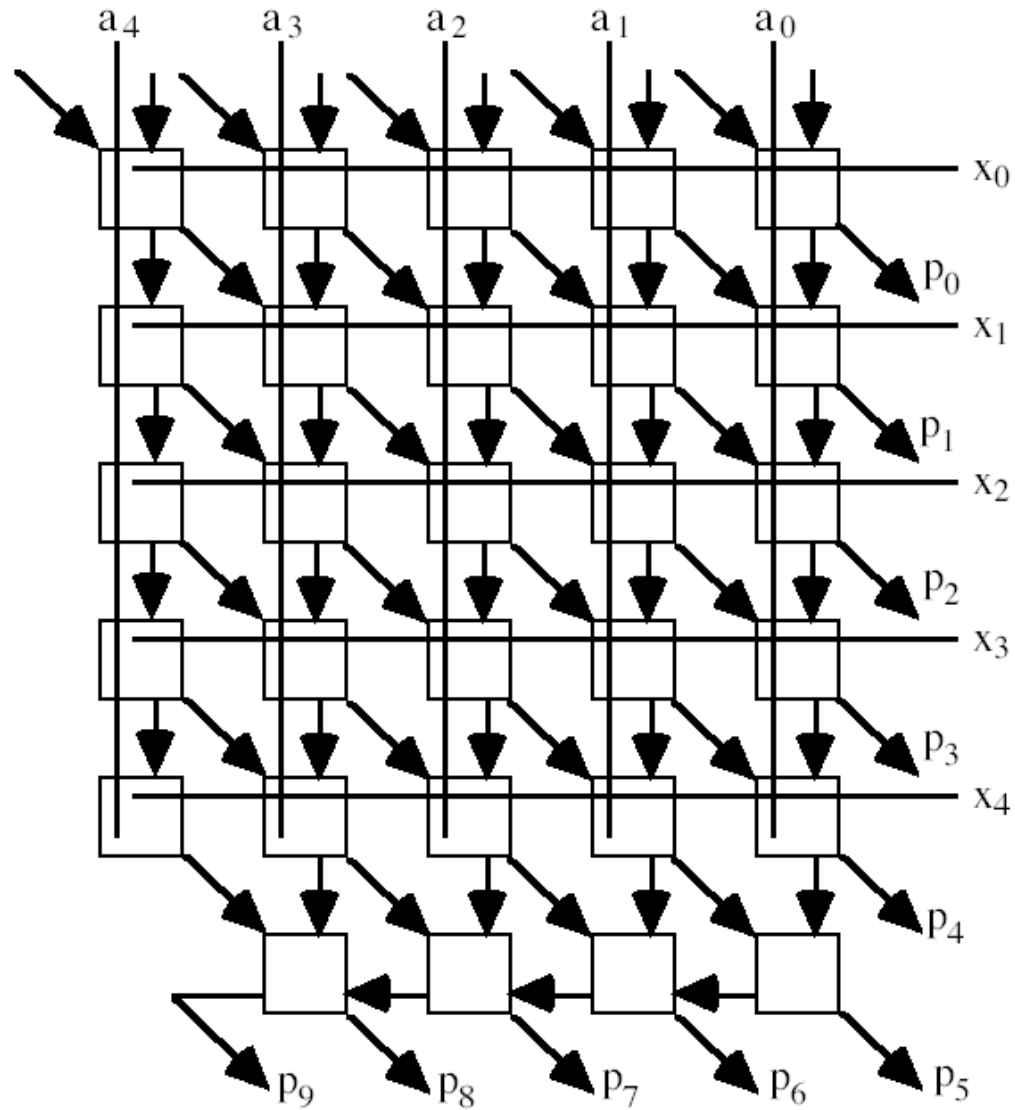5 x 5 Array Multiplier with modified cells



Pipelined 5 x 5 Multiplier

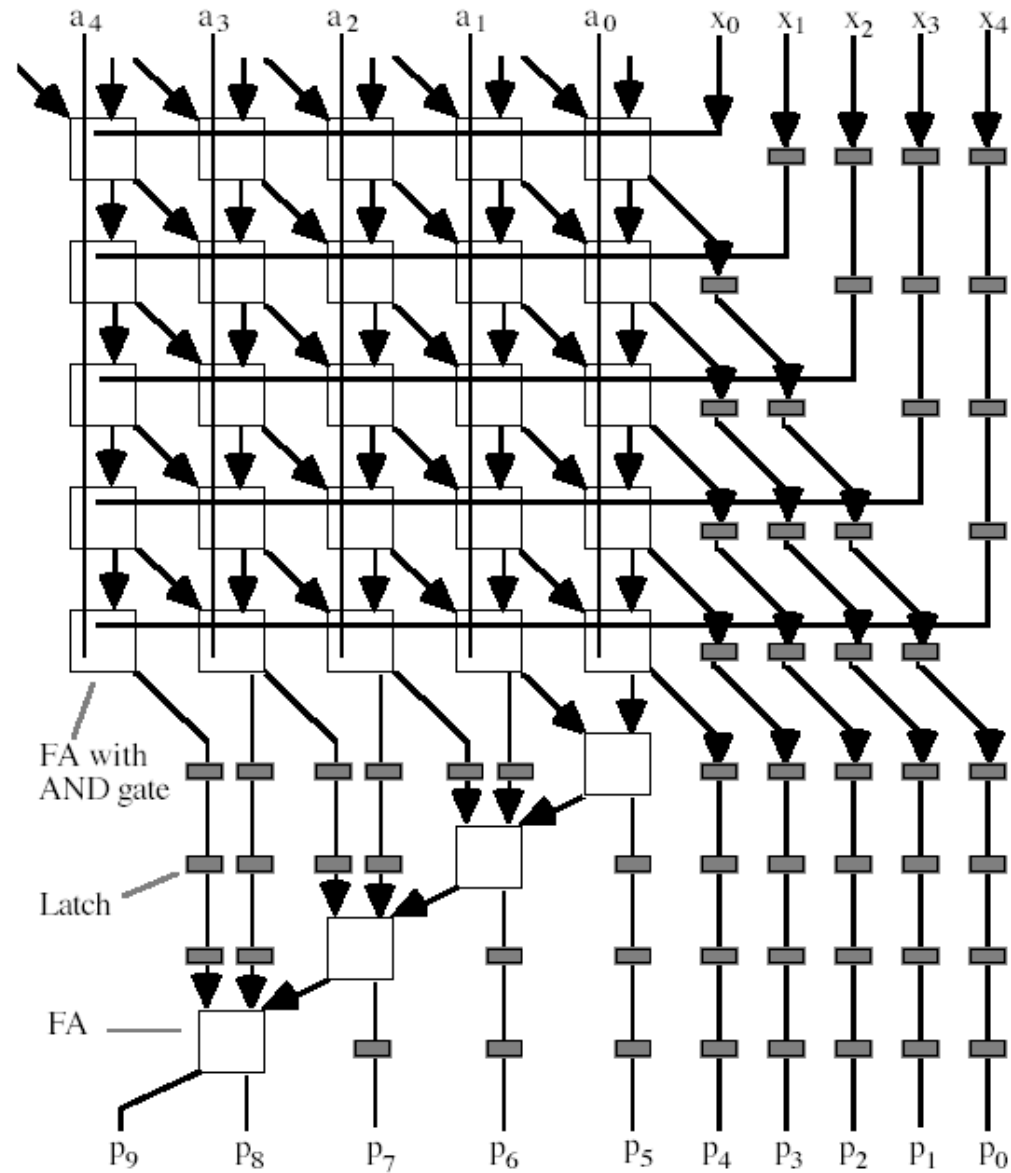

Optimizations for Squaring (1)

Multiply x by x

$$\begin{array}{cccccccccc}
 & & & & & x_4 & x_3 & x_2 & x_1 & x_0 \\
 & & & & & \times & x_4 & x_3 & x_2 & x_1 & x_0 \\
 \hline
 & & & & & & x_4x_0 & x_3x_0 & x_2x_0 & x_1x_0 & x_0x_0 \\
 & & & & x_4x_1 & & x_3x_1 & x_2x_1 & x_1x_1 & x_0x_1 & \text{Reduce} \\
 & & & x_4x_2 & x_3x_2 & & x_2x_2 & x_1x_2 & x_0x_2 & \text{Move} & \text{to } x_0 \\
 & & x_4x_3 & x_3x_3 & x_2x_3 & & x_1x_3 & x_0x_3 & & \text{to next} & \\
 & x_4x_4 & x_3x_4 & x_2x_4 & x_1x_4 & x_0x_4 & & & & \text{column} & \\
 \hline
 p_9 & p_8 & p_7 & p_6 & p_5 & p_4 & p_3 & p_2 & p_1 & p_0
 \end{array}$$

Reduce the bit matrix

$$\begin{array}{cccccccccc}
 & & & & & x_4 & x_3 & x_2 & x_1 & x_0 \\
 & & & & & \times & x_4 & x_3 & x_2 & x_1 & x_0 \\
 \hline
 & & x_4x_3 & x_4x_2 & x_4x_1 & x_4x_0 & x_3x_0 & x_2x_0 & x_1x_0 & - & x_0 \\
 & & x_4 & & x_3x_2 & x_3x_1 & x_2x_1 & & x_1 & & \\
 & & & & x_3 & & x_2 & & & & \\
 \hline
 p_9 & p_8 & p_7 & p_6 & p_5 & p_4 & p_3 & p_2 & 0 & x_0
 \end{array}$$

Optimizations for Squaring (2)

$$x_i x_j$$

$$x_j x_i$$

$$x_i x_j + x_i x_j = 2 x_i x_j$$

$$x_i x_j$$

$$x_i x_i = x_i$$

$$x_i x_j$$

$$x_i$$

$$x_i x_j$$

$$x_i \overline{x_j}$$

$$x_i x_j + x_i = 2 x_i x_j - x_i x_j + x_i =$$

$$= 2 x_i x_j + x_i (1 - x_j) =$$

$$= 2 x_i x_j + x_i \overline{x_j}$$

Squaring Using Look-Up Tables

for relatively small values k

input= a

output= a^2

0	0
1	1
2	4
3	9
4	16
	...
i	i^2
	...
2^k-1	$(2^k-1)^2$

2^k words $2k$ -bit each

Multiplication Using Squaring

$$a \cdot x = \frac{(a+x)^2 - (a-x)^2}{4}$$